 


# ELECTRIC CIRCUITS

ELEVENTH EDITION



# ELECTRIC CIRCUITS

ELEVENTH EDITION

James W. Nilsson

*Professor Emeritus  
Iowa State University*

Susan A. Riedel

*Marquette University*



330 Hudson Street, NY NY 10013

*Senior Vice President Courseware Portfolio Management, Engineering, Computer Science, Mathematics, Statistics, and Global Editions:* Marcia J. Horton  
*Director, Portfolio Management, Engineering, Computer Science, and Global Editions:* Julian Partridge  
*Specialist, Higher Ed Portfolio Management:* Norrin Dias  
*Portfolio Management Assistant:* Emily Egan  
*Managing Producer, ECS and Mathematics:* Scott Disanno  
*Senior Content Producer:* Erin Ault  
*Manager, Rights and Permissions:* Ben Ferrini  
*Operations Specialist:* Maura Zaldivar-Garcia

*Inventory Manager:* Ann Lam  
*Product Marketing Manager:* Yvonne Vannatta  
*Field Marketing Manager:* Demetrius Hall  
*Marketing Assistant:* Jon Bryant  
*Project Manager:* Rose Kernan  
*Cover Design:* Black Horse Designs  
*Cover Art:* © Leonardo Ulían, Matrix board series 06 - Resistance by abstraction, 2017.  
*Composition:* Integra Publishing Services  
*Cover Printer:* Phoenix Color/Hagerstown  
*Printer/Binder:* LSC Communications, Inc.

Credits and acknowledgments borrowed from other sources and reproduced, with permission, in this textbook appear on appropriate page within text.

---

**Copyright © 2019, 2015, 2008, 2005 Pearson Education, Inc., Hoboken, NJ 07030.** All rights reserved. Manufactured in the United States of America. This publication is protected by Copyright, and permission should be obtained from the publisher prior to any prohibited reproduction, storage in a retrieval system, or transmission in any form or by any means, electronic, mechanical, photocopying, recording, or otherwise. For information regarding permissions, request forms and the appropriate contacts within the Pearson Education Global Rights & Permissions department, please visit [www.pearsoned.com/permissions/](http://www.pearsoned.com/permissions/).

MATLAB is a registered trademark of The MathWorks, Inc., 3 Apple Hill Road, Natick, MA.

#### **Library of Congress Cataloging-in-Publication Data**

Names: Nilsson, James William, author. | Riedel, Susan A., author.  
Title: Electric circuits / James W. Nilsson, professor emeritus Iowa State University, Susan A. Riedel, Marquette University.  
Description: Eleventh edition. | Pearson, [2019] | Includes index.  
Identifiers: LCCN 2017025128 | ISBN 9780134746968 | ISBN 0134746961  
Subjects: LCSH: Electric circuits.  
Classification: LCC TK454 .N54 2019 | DDC 621.319/2—dc23  
LC record available at <https://lccn.loc.gov/2017025128>





Courtesy of Anna Nilsson

## In Memoriam

We remember our beloved author, James W. Nilsson, for his lasting legacy to the electrical and computer engineering field.

The first edition of *Electric Circuits* was published in 1983. As this book evolved over the years to better meet the needs of both students and their instructors, the underlying teaching methodologies Jim established remain relevant, even in the Eleventh Edition.

Jim earned his bachelor's degree at the University of Iowa (1948), and his master's degree (1952) and Ph.D. (1958) at Iowa State University. He joined the ISU faculty in 1948 and taught electrical engineering there for 39 years.

He became an IEEE fellow in 1990 and earned the prestigious IEEE Undergraduate Teaching Award in 1992.

For Anna



# Brief Contents

	List of Examples	xii
	List of Tables	xvi
	List of Analysis Methods	xvii
	Preface	xx
<b>Chapter 1</b>	Circuit Variables	2
<b>Chapter 2</b>	Circuit Elements	26
<b>Chapter 3</b>	Simple Resistive Circuits	58
<b>Chapter 4</b>	Techniques of Circuit Analysis	92
<b>Chapter 5</b>	The Operational Amplifier	150
<b>Chapter 6</b>	Inductance, Capacitance, and Mutual Inductance	182
<b>Chapter 7</b>	Response of First-Order $RL$ and $RC$ Circuits	220
<b>Chapter 8</b>	Natural and Step Responses of $RLC$ Circuits	272
<b>Chapter 9</b>	Sinusoidal Steady-State Analysis	318
<b>Chapter 10</b>	Sinusoidal Steady-State Power Calculations	374
<b>Chapter 11</b>	Balanced Three-Phase Circuits	412
<b>Chapter 12</b>	Introduction to the Laplace Transform	444
<b>Chapter 13</b>	The Laplace Transform in Circuit Analysis	482
<b>Chapter 14</b>	Introduction to Frequency Selective Circuits	536
<b>Chapter 15</b>	Active Filter Circuits	572
<b>Chapter 16</b>	Fourier Series	618
<b>Chapter 17</b>	The Fourier Transform	660
<b>Chapter 18</b>	Two-Port Circuits	692
<b>Appendix A</b>	The Solution of Linear Simultaneous Equations	718
<b>Appendix B</b>	Complex Numbers	727
<b>Appendix C</b>	More on Magnetically Coupled Coils and Ideal Transformers	733
<b>Appendix D</b>	The Decibel	741
<b>Appendix E</b>	Bode Diagrams	743
<b>Appendix F</b>	An Abbreviated Table of Trigonometric Identities	757
<b>Appendix G</b>	An Abbreviated Table of Integrals	758
<b>Appendix H</b>	Common Standard Component Values	760
	Answers to Selected Problems	761
	Index	771

# Contents

List of Examples xii

List of Tables xvi

List of Analysis Methods xvii

Preface xx

## Chapter 1 Circuit Variables 2

*Practical Perspective: Balancing Power* 3

1.1 Electrical Engineering: An Overview 4

1.2 The International System of Units 9

1.3 Circuit Analysis: An Overview 11

1.4 Voltage and Current 12

1.5 The Ideal Basic Circuit Element 14

1.6 Power and Energy 15

*Practical Perspective: Balancing Power* 18

*Summary* 19

*Problems* 20

## Chapter 2 Circuit Elements 26

*Practical Perspective: Heating with Electric Radiators* 27

2.1 Voltage and Current Sources 28

2.2 Electrical Resistance (Ohm's Law) 32

2.3 Constructing a Circuit Model 36

2.4 Kirchhoff's Laws 39

2.5 Analyzing a Circuit Containing Dependent Sources 45

*Practical Perspective: Heating with Electric Radiators* 48

*Summary* 50

*Problems* 50

## Chapter 3 Simple Resistive Circuits 58

*Practical Perspective: Resistive Touch Screens* 59

3.1 Resistors in Series 60

3.2 Resistors in Parallel 61

3.3 The Voltage-Divider and Current-Divider Circuits 64

3.4 Voltage Division and Current Division 68

3.5 Measuring Voltage and Current 70

3.6 Measuring Resistance—The Wheatstone Bridge 73

3.7 Delta-to-Wye (Pi-to-Tee) Equivalent Circuits 75

viii

*Practical Perspective: Resistive Touch*

*Screens* 78

*Summary* 79

*Problems* 80

## Chapter 4 Techniques of Circuit Analysis 92

*Practical Perspective: Circuits with Realistic Resistors* 93

4.1 Terminology 94

4.2 Introduction to the Node-Voltage Method 96

4.3 The Node-Voltage Method and Dependent Sources 98

4.4 The Node-Voltage Method: Some Special Cases 100

4.5 Introduction to the Mesh-Current Method 104

4.6 The Mesh-Current Method and Dependent Sources 107

4.7 The Mesh-Current Method: Some Special Cases 108

4.8 The Node-Voltage Method Versus the Mesh-Current Method 112

4.9 Source Transformations 115

4.10 Thévenin and Norton Equivalents 118

4.11 More on Deriving the Thévenin Equivalent 123

4.12 Maximum Power Transfer 126

4.13 Superposition 129

*Practical Perspective: Circuits with Realistic Resistors* 131

*Summary* 134

*Problems* 136

## Chapter 5 The Operational Amplifier 150

*Practical Perspective: Strain Gages* 151

5.1 Operational Amplifier Terminals 152

5.2 Terminal Voltages and Currents 152

5.3 The Inverting-Amplifier Circuit 156

5.4 The Summing-Amplifier Circuit 158

5.5 The Noninverting-Amplifier Circuit 160

5.6 The Difference-Amplifier Circuit 162

5.7 A More Realistic Model for the Operational Amplifier 167

*Practical Perspective: Strain Gages* 171

*Summary* 172

*Problems* 173



## Chapter 6 Inductance, Capacitance, and Mutual Inductance 182

*Practical Perspective: Capacitive Touch Screens* 183

- 6.1 The Inductor 184
  - 6.2 The Capacitor 189
  - 6.3 Series-Parallel Combinations of Inductance and Capacitance 194
  - 6.4 Mutual Inductance 199
  - 6.5 A Closer Look at Mutual Inductance 203
- Practical Perspective: Capacitive Touch Screens* 209
- Summary* 211
- Problems* 212

## Chapter 7 Response of First-Order $RL$ and $RC$ Circuits 220

*Practical Perspective: Artificial Pacemaker* 221

- 7.1 The Natural Response of an  $RL$  Circuit 222
  - 7.2 The Natural Response of an  $RC$  Circuit 228
  - 7.3 The Step Response of  $RL$  and  $RC$  Circuits 233
  - 7.4 A General Solution for Step and Natural Responses 241
  - 7.5 Sequential Switching 246
  - 7.6 Unbounded Response 250
  - 7.7 The Integrating Amplifier 252
- Practical Perspective: Artificial Pacemaker* 255
- Summary* 256
- Problems* 256

## Chapter 8 Natural and Step Responses of $RLC$ Circuits 272

*Practical Perspective: Clock for Computer Timing* 273

- 8.1 Introduction to the Natural Response of a Parallel  $RLC$  Circuit 274
  - 8.2 The Forms of the Natural Response of a Parallel  $RLC$  Circuit 278
  - 8.3 The Step Response of a Parallel  $RLC$  Circuit 289
  - 8.4 The Natural and Step Response of a Series  $RLC$  Circuit 296
  - 8.5 A Circuit with Two Integrating Amplifiers 303
- Practical Perspective: Clock for Computer Timing* 308
- Summary* 309
- Problems* 310

## Chapter 9 Sinusoidal Steady-State Analysis 318

*Practical Perspective: A Household Distribution Circuit* 319

- 9.1 The Sinusoidal Source 320
  - 9.2 The Sinusoidal Response 323
  - 9.3 The Phasor 324
  - 9.4 The Passive Circuit Elements in the Frequency Domain 327
  - 9.5 Kirchhoff's Laws in the Frequency Domain 332
  - 9.6 Series, Parallel, and Delta-to-Wye Simplifications 333
  - 9.7 Source Transformations and Thévenin–Norton Equivalent Circuits 340
  - 9.8 The Node-Voltage Method 344
  - 9.9 The Mesh-Current Method 345
  - 9.10 The Transformer 347
  - 9.11 The Ideal Transformer 351
  - 9.12 Phasor Diagrams 357
- Practical Perspective: A Household Distribution Circuit* 359
- Summary* 361
- Problems* 362

## Chapter 10 Sinusoidal Steady-State Power Calculations 374

*Practical Perspective: Vampire Power* 375

- 10.1 Instantaneous Power 376
  - 10.2 Average and Reactive Power 377
  - 10.3 The rms Value and Power Calculations 382
  - 10.4 Complex Power 384
  - 10.5 Power Calculations 386
  - 10.6 Maximum Power Transfer 393
- Practical Perspective: Vampire Power* 399
- Summary* 401
- Problems* 401

## Chapter 11 Balanced Three-Phase Circuits 412

*Practical Perspective: Transmission and Distribution of Electric Power* 413

- 11.1 Balanced Three-Phase Voltages 414
  - 11.2 Three-Phase Voltage Sources 415
  - 11.3 Analysis of the Wye-Wye Circuit 416
  - 11.4 Analysis of the Wye-Delta Circuit 422
  - 11.5 Power Calculations in Balanced Three-Phase Circuits 425
  - 11.6 Measuring Average Power in Three-Phase Circuits 430
- Practical Perspective: Transmission and Distribution of Electric Power* 433
- Summary* 435
- Problems* 436

## Chapter 12 Introduction to the Laplace Transform 444

*Practical Perspective: Transient Effects* 445

- 12.1 Definition of the Laplace Transform 446
- 12.2 The Step Function 447
- 12.3 The Impulse Function 449
- 12.4 Functional Transforms 452
- 12.5 Operational Transforms 453
- 12.6 Applying the Laplace Transform 458
- 12.7 Inverse Transforms 460
- 12.8 Poles and Zeros of  $F(s)$  470
- 12.9 Initial- and Final-Value Theorems 472
- Practical Perspective: Transient Effects* 474
- Summary* 476
- Problems* 477

## Chapter 13 The Laplace Transform in Circuit Analysis 482

*Practical Perspective: Surge Suppressors* 483

- 13.1 Circuit Elements in the  $s$  Domain 484
- 13.2 Circuit Analysis in the  $s$  Domain 486
- 13.3 Applications 488
- 13.4 The Transfer Function 500
- 13.5 The Transfer Function in Partial Fraction Expansions 502
- 13.6 The Transfer Function and the Convolution Integral 505
- 13.7 The Transfer Function and the Steady-State Sinusoidal Response 511
- 13.8 The Impulse Function in Circuit Analysis 514
- Practical Perspective: Surge Suppressors* 520
- Summary* 521
- Problems* 522

## Chapter 14 Introduction to Frequency Selective Circuits 536

*Practical Perspective: Pushbutton Telephone Circuits* 537

- 14.1 Some Preliminaries 538
- 14.2 Low-Pass Filters 539
- 14.3 High-Pass Filters 545
- 14.4 Bandpass Filters 550
- 14.5 Bandreject Filters 560
- Practical Perspective: Pushbutton Telephone Circuits* 564
- Summary* 564
- Problems* 565

## Chapter 15 Active Filter Circuits 572

*Practical Perspective: Bass Volume Control* 573

- 15.1 First-Order Low-Pass and High-Pass Filters 574
- 15.2 Scaling 577
- 15.3 Op Amp Bandpass and Bandreject Filters 580
- 15.4 Higher-Order Op Amp Filters 587
- 15.5 Narrowband Bandpass and Bandreject Filters 600
- Practical Perspective: Bass Volume Control* 605
- Summary* 608
- Problems* 609

## Chapter 16 Fourier Series 618

*Practical Perspective: Active High-Q Filters* 619

- 16.1 Fourier Series Analysis: An Overview 621
- 16.2 The Fourier Coefficients 622
- 16.3 The Effect of Symmetry on the Fourier Coefficients 625
- 16.4 An Alternative Trigonometric Form of the Fourier Series 631
- 16.5 An Application 633
- 16.6 Average-Power Calculations with Periodic Functions 639
- 16.7 The rms Value of a Periodic Function 641
- 16.8 The Exponential Form of the Fourier Series 642
- 16.9 Amplitude and Phase Spectra 645
- Practical Perspective: Active High-Q Filters* 647
- Summary* 649
- Problems* 650

## Chapter 17 The Fourier Transform 660

*Practical Perspective: Filtering Digital Signals* 661

- 17.1 The Derivation of the Fourier Transform 662
- 17.2 The Convergence of the Fourier Integral 664
- 17.3 Using Laplace Transforms to Find Fourier Transforms 666
- 17.4 Fourier Transforms in the Limit 668
- 17.5 Some Mathematical Properties 671
- 17.6 Operational Transforms 672
- 17.7 Circuit Applications 677
- 17.8 Parseval's Theorem 679
- Practical Perspective: Filtering Digital Signals* 685
- Summary* 686
- Problems* 686

**Chapter 18 Two-Port Circuits 692**

*Practical Perspective: Characterizing  
an Unknown Circuit 693*

- 18.1** The Terminal Equations 694
- 18.2** The Two-Port Parameters 695
- 18.3** Analysis of the Terminated  
Two-Port Circuit 703
- 18.4** Interconnected Two-Port Circuits 708  
*Practical Perspective: Characterizing  
an Unknown Circuit 711*  
*Summary 712*  
*Problems 713*

**Appendix A The Solution of Linear  
Simultaneous  
Equations 718**

- A.1 Preliminary Steps 718
- A.2 Calculator and Computer Methods 719
- A.3 Paper-and-Pencil Methods 721
- A.4 Applications 723

**Appendix B Complex Numbers 727**

- B.1 Notation 727
- B.2 The Graphical Representation of a Complex  
Number 728
- B.3 Arithmetic Operations 729
- B.4 Useful Identities 730
- B.5 The Integer Power of a Complex Number 731
- B.6 The Roots of a Complex Number 731

**Appendix C More on Magnetically  
Coupled Coils and Ideal  
Transformers 733**

- C.1 Equivalent Circuits for Magnetically  
Coupled Coils 733

- C.2 The Need for Ideal Transformers  
in the Equivalent Circuits 737

**Appendix D The Decibel 741****Appendix E Bode Diagrams 743**

- E.1 Real, First-Order Poles and Zeros 743
- E.2 Straight-Line Amplitude Plots 744
- E.3 More Accurate Amplitude Plots 747
- E.4 Straight-Line Phase Angle Plots 748
- E.5 Bode Diagrams: Complex Poles and Zeros 750
- E.6 Straight-Line Amplitude Plots for Complex  
Poles 751
- E.7 Correcting Straight-Line Amplitude Plots for  
Complex Poles 752
- E.8 Phase Angle Plots for Complex Poles 754

**Appendix F An Abbreviated Table  
of Trigonometric  
Identities 757****Appendix G An Abbreviated Table of  
Integrals 758****Appendix H Common Standard  
Component Values 760****Answers to Selected Problems 761****Index 771**

# List of Examples

## Chapter 1

- 1.1 Using SI Units and Prefixes for Powers of 10 11
- 1.2 Relating Current and Charge 15
- 1.3 Using the Passive Sign Convention 17
- 1.4 Relating Voltage, Current, Power, and Energy 17

## Chapter 2

- 2.1 Testing Interconnections of Ideal Sources 30
- 2.2 Testing Interconnections of Ideal Independent and Dependent Sources 31
- 2.3 Calculating Voltage, Current, and Power for a Simple Resistive Circuit 34
- 2.4 Constructing a Circuit Model of a Flashlight 36
- 2.5 Constructing a Circuit Model Based on Terminal Measurements 38
- 2.6 Using Kirchhoff's Current Law 41
- 2.7 Using Kirchhoff's Voltage Law 42
- 2.8 Applying Ohm's Law and Kirchhoff's Laws to Find an Unknown Current 42
- 2.9 Constructing a Circuit Model Based on Terminal Measurements 43
- 2.10 Analyzing a Circuit with a Dependent Source 45
- 2.11 Applying Ohm's Law and Kirchhoff's Laws to Find an Unknown Voltage 46
- 2.12 Applying Ohm's Law and Kirchhoff's Law in an Amplifier Circuit 47

## Chapter 3

- 3.1 Applying Series-Parallel Simplification 62
- 3.2 Solving a Circuit Using Series-Parallel Simplification 63
- 3.3 Designing a Simple Voltage Divider 65
- 3.4 Adding a Resistive Load to a Voltage Divider 65
- 3.5 The Effect of Resistor Tolerance on the Voltage-Divider Circuit 66
- 3.6 Designing a Current-Divider Circuit 67
- 3.7 Using Voltage Division and Current Division to Solve a Circuit 69
- 3.8 Using a d'Arsonval Ammeter 71
- 3.9 Using a d'Arsonval Voltmeter 72
- 3.10 Using a Wheatstone Bridge to Measure Resistance 75
- 3.11 Applying a Delta-to-Wye Transform 77

## Chapter 4

- 4.1 Identifying Node, Branch, Mesh, and Loop in a Circuit 94

- 4.2 Using Essential Nodes and Essential Branches to Write Simultaneous Equations 95
- 4.3 Using the Node-Voltage Method 97
- 4.4 Using the Node-Voltage Method with Dependent Sources 99
- 4.5 Node-Voltage Analysis of the Amplifier Circuit 102
- 4.6 Using the Mesh-Current Method 106
- 4.7 Using the Mesh-Current Method with Dependent Sources 107
- 4.8 A Special Case in the Mesh-Current Method 108
- 4.9 Mesh-Current Analysis of the Amplifier Circuit 111
- 4.10 Understanding the Node-Voltage Method Versus Mesh-Current Method 113
- 4.11 Comparing the Node-Voltage and Mesh-Current Methods 114
- 4.12 Using Source Transformations to Solve a Circuit 116
- 4.13 Using Special Source Transformation Techniques 117
- 4.14 Finding a Thévenin Equivalent 120
- 4.15 Finding a Norton Equivalent 121
- 4.16 Finding the Thévenin Equivalent of a Circuit with a Dependent Source 122
- 4.17 Finding the Thévenin Equivalent Resistance Directly from the Circuit 123
- 4.18 Finding the Thévenin Equivalent Resistance Using a Test Source 124
- 4.19 Finding the Thévenin Equivalent of a Circuit with Dependent Sources and Resistors 124
- 4.20 Using a Thévenin Equivalent to Analyze the Amplifier Circuit 125
- 4.21 Calculating the Condition for Maximum Power Transfer 127
- 4.22 Using Superposition to Solve a Circuit 129
- 4.23 Using Superposition to Solve a Circuit with Dependent Sources 130

## Chapter 5

- 5.1 Analyzing an Op Amp Circuit 155
- 5.2 Designing an Inverting Amplifier 157
- 5.3 Designing a Summing Amplifier 159
- 5.4 Designing a Noninverting Amplifier 161
- 5.5 Designing a Difference Amplifier 163
- 5.6 Calculating the CMRR 167
- 5.7 Analyzing a Noninverting-Amplifier Circuit using a Realistic Op Amp Model 169

## Chapter 6

- 6.1** Determining the Voltage, Given the Current, at the Terminals of an Inductor 184
- 6.2** Determining the Current, Given the Voltage, at the Terminals of an Inductor 186
- 6.3** Determining the Current, Voltage, Power, and Energy for an Inductor 187
- 6.4** Determining Current, Voltage, Power, and Energy for a Capacitor 191
- 6.5** Finding  $v$ ,  $p$ , and  $w$  Induced by a Triangular Current Pulse for a Capacitor 192
- 6.6** Finding the Equivalent Inductance 196
- 6.7** Finding the Equivalent Capacitance 197
- 6.8** Finding Mesh-Current Equations for a Circuit with Magnetically Coupled Coils 201
- 6.9** Calculating the Coupling Coefficient and Stored Energy for Magnetically Coupled Coils 209

## Chapter 7

- 7.1** Determining the Natural Response of an  $RL$  Circuit 224
- 7.2** Determining the Natural Response of an  $RL$  Circuit with Parallel Inductors 227
- 7.3** Determining the Natural Response of an  $RC$  Circuit 230
- 7.4** Determining the Natural Response of an  $RC$  Circuit with Series Capacitors 231
- 7.5** Determining the Step Response of an  $RL$  Circuit 234
- 7.6** Determining the Step Response of an  $RC$  Circuit 239
- 7.7** Using the General Solution Method to Find an  $RL$  Circuit's Natural Response 242
- 7.8** Using the General Solution Method to Find an  $RC$  Circuit's Step Response 243
- 7.9** Using the General Solution Method to Find an  $RL$  Circuit's Step Response 244
- 7.10** Determining the Step Response of a Circuit with Magnetically Coupled Coils 245
- 7.11** Analyzing an  $RL$  Circuit that has Sequential Switching 247
- 7.12** Analyzing an  $RC$  Circuit that has Sequential Switching 249
- 7.13** Finding the Unbounded Response in an  $RC$  Circuit 251
- 7.14** Analyzing an Integrating Amplifier 253
- 7.15** Analyzing an Integrating Amplifier that has Sequential Switching 253

## Chapter 8

- 8.1** Finding the Roots of the Characteristic Equation of a Parallel  $RLC$  Circuit 277

- 8.2** Finding the Overdamped Natural Response of a Parallel  $RLC$  Circuit 280
- 8.3** Calculating Branch Currents in the Natural Response of a Parallel  $RLC$  Circuit 281
- 8.4** Finding the Underdamped Natural Response of a Parallel  $RLC$  Circuit 284
- 8.5** Finding the Critically Damped Natural Response of a Parallel  $RLC$  Circuit 288
- 8.6** Finding the Overdamped Step Response of a Parallel  $RLC$  Circuit 293
- 8.7** Finding the Underdamped Step Response of a Parallel  $RLC$  Circuit 294
- 8.8** Finding the Critically Damped Step Response of a Parallel  $RLC$  Circuit 294
- 8.9** Comparing the Three-Step Response Forms 295
- 8.10** Finding Step Response of a Parallel  $RLC$  Circuit with Initial Stored Energy 295
- 8.11** Finding the Natural Response of a Series  $RLC$  Circuit 302
- 8.12** Finding the Step Response of a Series  $RLC$  Circuit 302
- 8.13** Analyzing Two Cascaded Integrating Amplifiers 305
- 8.14** Analyzing Two Cascaded Integrating Amplifiers with Feedback Resistors 307

## Chapter 9

- 9.1** Finding the Characteristics of a Sinusoidal Current 321
- 9.2** Finding the Characteristics of a Sinusoidal Voltage 322
- 9.3** Translating a Sine Expression to a Cosine Expression 322
- 9.4** Calculating the rms Value of a Triangular Waveform 322
- 9.5** Adding Cosines Using Phasors 326
- 9.6** Calculating Component Voltages Using Phasor Techniques 331
- 9.7** Using KVL in the Frequency Domain 333
- 9.8** Combining Impedances in Series 334
- 9.9** Combining Impedances in Series and in Parallel 337
- 9.10** Using a Delta-to-Wye Transform in the Frequency Domain 339
- 9.11** Performing Source Transformations in the Frequency Domain 341
- 9.12** Finding a Thévenin Equivalent in the Frequency Domain 342
- 9.13** Using the Node-Voltage Method in the Frequency Domain 344
- 9.14** Using the Mesh-Current Method in the Frequency Domain 346



- 9.15** Analyzing a Linear Transformer in the Frequency Domain 349
- 9.16** Analyzing an Ideal Transformer Circuit in the Frequency Domain 355
- 9.17** Using Phasor Diagrams to Analyze a Circuit 357
- 9.18** Using Phasor Diagrams to Analyze Capacitive Loading Effects 358

## Chapter 10

- 10.1** Calculating Average and Reactive Power 380
- 10.2** Making Power Calculations Involving Household Appliances 382
- 10.3** Determining Average Power Delivered to a Resistor by a Sinusoidal Voltage 384
- 10.4** Calculating Complex Power 385
- 10.5** Calculating Power Using Phasor Voltage and Current 387
- 10.6** Calculating Average and Reactive Power 389
- 10.7** Calculating Power in Parallel Loads 390
- 10.8** Balancing Power Delivered with Power Absorbed in an AC Circuit 391
- 10.9** Determining Maximum Power Transfer without Load Restrictions 395
- 10.10** Determining Maximum Power Transfer with Load Impedance Restriction 396
- 10.11** Finding Maximum Power Transfer with Impedance Angle Restrictions 396
- 10.12** Finding Maximum Power Transfer in a Circuit with an Ideal Transformer 397

## Chapter 11

- 11.1** Analyzing a Wye-Wye Circuit 420
- 11.2** Analyzing a Wye-Delta Circuit 423
- 11.3** Calculating Power in a Three-Phase Wye-Wye Circuit 428
- 11.4** Calculating Power in a Three-Phase Wye-Delta Circuit 428
- 11.5** Calculating Three-Phase Power with an Unspecified Load 429
- 11.6** Computing Wattmeter Readings in Three-Phase Circuits 432

## Chapter 12

- 12.1** Using Step Functions to Represent a Function of Finite Duration 448
- 12.2** Using Laplace Transforms to Predict a Circuit's Response 460
- 12.3** Finding the Inverse Laplace Transform when  $F(s)$  has Distinct Real Roots 462
- 12.4** Finding the Inverse Laplace Transform when  $F(s)$  has Distinct Complex Roots 465
- 12.5** Finding the Inverse Laplace Transform when  $F(s)$  has Repeated Real Roots 467

- 12.6** Finding the Inverse Laplace Transform when  $F(s)$  has Repeated Complex Roots 468
- 12.7** Finding the Inverse Laplace Transform of an Improper Rational Function 470
- 12.8** Finding and Plotting the Poles and Zeros of an  $s$ -Domain Function 471
- 12.9** Applying the Initial- and Final-Value Theorems 474

## Chapter 13

- 13.1** Transforming a Circuit into the  $s$  Domain 488
- 13.2** The Natural Response of an  $RC$  Circuit 489
- 13.3** The Step Response of an  $RLC$  Circuit 489
- 13.4** Analyzing a Circuit with a Sinusoidal Source 491
- 13.5** Analyzing a Circuit with Multiple Meshes 493
- 13.6** Creating a Thévenin Equivalent in the  $s$  Domain 495
- 13.7** Analyzing a Circuit with Mutual Inductance 497
- 13.8** Applying Superposition in the  $s$  Domain 499
- 13.9** Deriving the Transfer Function of a Circuit 501
- 13.10** Analyzing the Transfer Function of a Circuit 503
- 13.11** Using the Convolution Integral to Find an Output Signal 509
- 13.12** Using the Transfer Function to Find the Steady-State Sinusoidal Response 513
- 13.13** A Series Inductor Circuit with an Impulsive Response 515
- 13.14** A Circuit with Both Internally Generated and Externally Applied Impulses 518

## Chapter 14

- 14.1** Designing a Low-Pass Filter 543
- 14.2** Designing a Series  $RC$  Low-Pass Filter 544
- 14.3** Designing a Series  $RL$  High-Pass Filter 547
- 14.4** Loading the Series  $RL$  High-Pass Filter 548
- 14.5** Designing a Bandpass Filter 555
- 14.6** Designing a Parallel  $RLC$  Bandpass Filter 555
- 14.7** Determining Effect of a Nonideal Voltage Source on a  $RLC$  Bandpass Filter 557
- 14.8** Designing a Series  $RLC$  Bandreject Filter 562

## Chapter 15

- 15.1** Designing a Low-Pass Op Amp Filter 575
- 15.2** Designing a High-Pass Op Amp Filter 576
- 15.3** Scaling a Series  $RLC$  Filter 578
- 15.4** Scaling a Prototype Low-Pass Op Amp Filter 579
- 15.5** Designing a Broadband Bandpass Op Amp Filter 583
- 15.6** Designing a Broadband Bandreject Op Amp Filter 586

- 15.7** Designing a Fourth-Order Low-Pass Active Filter 589
- 15.8** Calculating Butterworth Transfer Functions 592
- 15.9** Designing a Fourth-Order Low-Pass Butterworth Filter 594
- 15.10** Determining the Order of a Butterworth Filter 597
- 15.11** An Alternate Approach to Determining the Order of a Butterworth Filter 597
- 15.12** Designing a Butterworth Bandpass Filter 599
- 15.13** Designing a High-Q Bandpass Filter 602
- 15.14** Designing a High-Q Bandreject Filter 604

## Chapter 16

- 16.1** Finding the Fourier Series of a Triangular Waveform 623
- 16.2** Finding the Fourier Series of a Periodic Function with Symmetry 630
- 16.3** Calculating Forms of the Trigonometric Fourier Series for Periodic Voltage 632
- 16.4** Finding the Response of an *RLC* Circuit to a Square-Wave Voltage 637
- 16.5** Calculating Average Power for a Circuit with a Periodic Voltage Source 640
- 16.6** Estimating the rms Value of a Periodic Function 642
- 16.7** Finding the Exponential Form of the Fourier Series 644
- 16.8** Plotting the Amplitude and Phase Spectra for a Periodic Voltage 646

## Chapter 17

- 17.1** Finding the Fourier Transform of a Constant 665
- 17.2** Finding the Fourier Transform from the Laplace Transform 667
- 17.3** Deriving an Operational Fourier Transform 675
- 17.4** Using the Fourier Transform to Find the Transient Response 677
- 17.5** Using the Fourier Transform to Find the Sinusoidal Steady-State Response 678
- 17.6** Applying Parseval's Theorem 681
- 17.7** Applying Parseval's Theorem to an Ideal Bandpass Filter 682
- 17.8** Applying Parseval's Theorem to a Low-Pass Filter 683
- 17.9** Calculating Energy Contained in a Rectangular Voltage Pulse 684

## Chapter 18

- 18.1** Finding the *z* Parameters of a Two-Port Circuit 696
- 18.2** Finding the *a* Parameters from Measurements 697
- 18.3** Finding *h* Parameters from Measurements and Table 18.1 700
- 18.4** Determining Whether a Circuit Is Reciprocal and Symmetric 701
- 18.5** Analyzing a Terminated Two-Port Circuit 707
- 18.6** Analyzing Cascaded Two-Port Circuits 710

# List of Tables

- |            |  |     |             |  |     |
|------------|--|-----|-------------|--|-----|
| <b>1.1</b> | The International System of Units (SI)                                       | 10  | <b>9.2</b>  | Admittance and Susceptance Values  | 336 |
| <b>1.2</b> | Derived Units in SI  | 10  | <b>9.3</b>  | Impedance and Related Values   | 361 |
| <b>1.3</b> | Standardized Prefixes to Signify Powers of 10                                | 10  | <b>10.1</b> | Annual Energy Requirements of Electric Household Appliances                              | 381 |
| <b>1.4</b> | Interpretation of Reference Directions in Fig. 1.5                           | 14  | <b>10.2</b> | Three Power Quantities and Their Units   | 385 |
| <b>1.5</b> | Voltage and Current Values for the Circuit in Fig. 1.7                       | 19  | <b>10.3</b> | Average Power Consumption of Common Electrical Devices                                   | 399 |
| <b>4.1</b> | Terms for Describing Circuits  | 95  | <b>12.1</b> | An Abbreviated List of Laplace Transform Pairs   | 453 |
| <b>4.2</b> | PSpice Sensitivity Analysis Results  | 133 | <b>12.2</b> | An Abbreviated List of Operational Transforms  | 458 |
| <b>4.3</b> | Steps in the Node-Voltage Method and the Mesh-Current Method                 | 135 | <b>12.3</b> | Four Useful Transform Pairs  | 469 |
| <b>6.1</b> | Inductor and Capacitor Duality   | 198 | <b>13.1</b> | Summary of the s-Domain Equivalent Circuits  | 486 |
| <b>7.1</b> | Value of $e^{-t/\tau}$ For $t$ Equal to Integral Multiples of $\tau$         | 226 | <b>14.1</b> | Input and Output Voltage Magnitudes for Several Frequencies                              | 543 |
| <b>8.1</b> | Natural-Response Parameters of the Parallel <i>RLC</i> Circuit               | 276 | <b>15.1</b> | Normalized (so that $\omega_c = 1$ rad/s) Butterworth Polynomials up to the Eighth Order | 593 |
| <b>8.2</b> | Equations for Analyzing the Natural Response of Parallel <i>RLC</i> Circuits | 288 | <b>17.1</b> | Fourier Transforms of Elementary Functions   | 670 |
| <b>8.3</b> | Equations for Analyzing the Step Response of Parallel <i>RLC</i> Circuits    | 293 | <b>17.2</b> | Operational Transforms   | 675 |
| <b>8.4</b> | Equations for Analyzing the Natural Response of Series <i>RLC</i> Circuits   | 299 | <b>18.1</b> | Parameter Conversion Table   | 699 |
| <b>8.5</b> | Equations for Analyzing the Step Response of Series <i>RLC</i> Circuits      | 301 | <b>18.2</b> | Two-Port Parameter Relationships for Reciprocal Circuits                                 | 701 |
| <b>9.1</b> | Impedance and Reactance Values   | 331 | <b>18.3</b> | Terminated Two-Port Equations  | 704 |




# List of Analysis Methods

<b>Analysis Method 4.1:</b>	The Basic Version of the Node-Voltage Method	97	<b>Analysis Method 7.4:</b>	Finding the <i>RC</i> Step Response	238
<b>Analysis Method 4.2:</b>	Modified Step 3 for the Node-Voltage Method	99	<b>Analysis Method 7.5:</b>	Finding the <i>RL</i> and <i>RC</i> Natural and Step Response	242
<b>Analysis Method 4.3:</b>	Complete Form of the Node-Voltage Method	102	<b>Analysis Method 8.1:</b>	The Natural Response of an Overdamped Parallel <i>RLC</i> Circuit	280
<b>Analysis Method 4.4:</b>	The Basic Version of the Mesh-Current Method	105	<b>Analysis Method 8.2:</b>	The Natural Response of an Overdamped or Underdamped Parallel <i>RLC</i> Circuit	283
<b>Analysis Method 4.5:</b>	Modified Step 3 for the Mesh-Current Method	107	<b>Analysis Method 8.3:</b>	The Natural Response of Parallel <i>RLC</i> Circuits	287
<b>Analysis Method 4.6:</b>	Complete Form of the Mesh-Current Method	110	<b>Analysis Method 8.4:</b>	The Step Response of Parallel <i>RLC</i> Circuits	292
<b>Analysis Method 5.1:</b>	Analyzing an Ideal Op Amp Circuit with a Negative Feedback Path	154	<b>Analysis Method 8.5:</b>	The Natural Response of Series <i>RLC</i> Circuits	299
<b>Analysis Method 7.1:</b>	Finding the <i>RL</i> Natural Response	224	<b>Analysis Method 8.6:</b>	The Step Response of Series <i>RLC</i> Circuits	301
<b>Analysis Method 7.2:</b>	Finding the <i>RC</i> Natural Response	230	<b>Analysis Method 13.1:</b>	Laplace-Transform Circuit Analysis Method	487
<b>Analysis Method 7.3:</b>	Finding the <i>RL</i> Step Response	234			


# Combine this...

## PART A

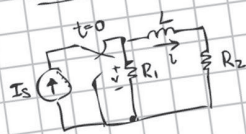

Given:  
 $I_s = 51.0 \text{ mA}$   
 $R_1 = 54.0 \text{ k}\Omega$   
 $R_2 = 51.0 \text{ k}\Omega$   
 $L = 51.0 \text{ mH}$

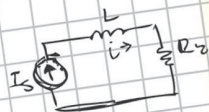Find:  
 initial current  $i(0^-)$   
 before break switch



$$I_s = i$$

$$i = 51.0 \text{ mA}$$

Assume when circuit is in steady state, inductor acts as a short



Use Kirchhoff's current law

$$I_s = i + i_R$$

$$I_s = i + \frac{V}{R}$$

$$I_s = i + \frac{i R_1}{R_2}$$


$$I_s = i \left( 1 + \frac{R_1}{R_2} \right)$$

$$\frac{I_s}{\left( 1 + \frac{R_1}{R_2} \right)} = i$$

$$i = \frac{51.0 \text{ mA}}{\left( 1 + \frac{54.0 \text{ k}\Omega}{51.0 \text{ k}\Omega} \right)} = 24.77 \text{ mA}$$
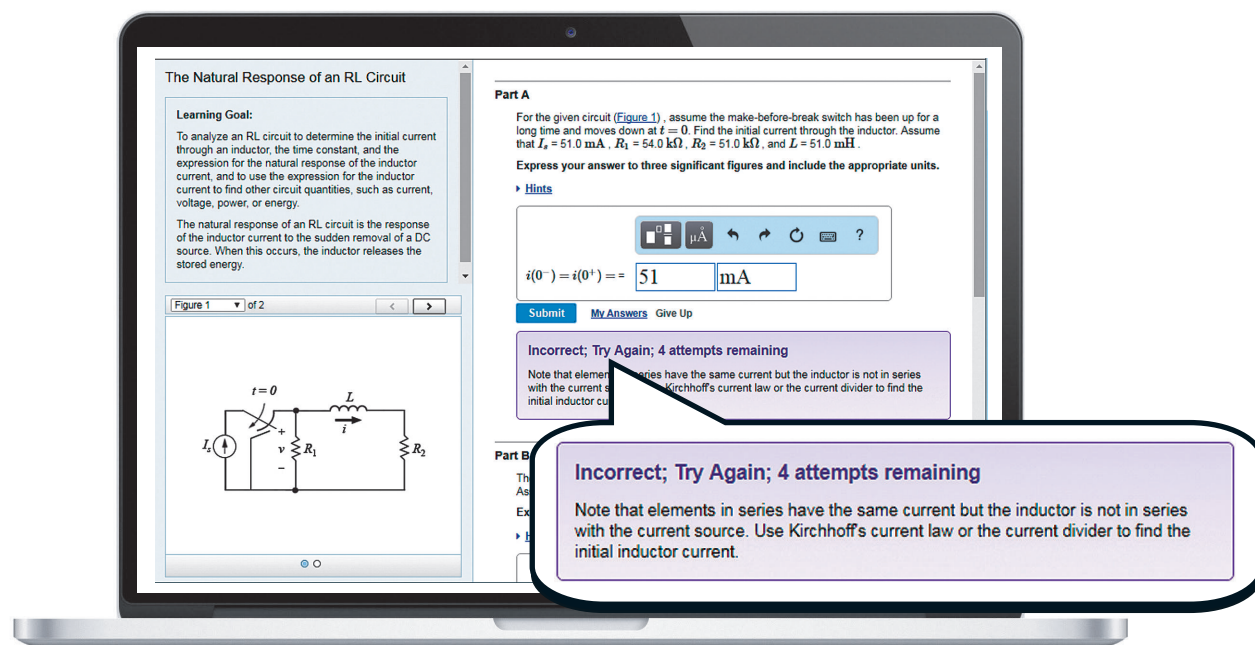
## With the Power of Mastering Engineering for Electric Circuits 11/e

Mastering is the teaching and learning platform that empowers every student. By combining trusted authors' content with digital tools developed to engage students and emulate the office hours experience, Mastering personalizes learning and improves results for each student.



## Empower each learner

Each student learns at a different pace. Personalized learning, including adaptive tools and wrong-answer feedback, pinpoints the precise areas where each student needs practice, giving all students the support they need — when and where they need it — to be successful.

Learn more at [www.pearson.com/mastering/engineering](http://www.pearson.com/mastering/engineering)

# Preface

The Eleventh Edition of *Electric Circuits* represents the most extensive revision to the text since the Fifth Edition, published in 1996. Every sentence, paragraph, subsection, and chapter has been examined to improve clarity, readability, and pedagogy. Yet the fundamental goals of the text are unchanged. These goals are:

- To build new concepts and ideas on concepts previously presented. This challenges students to see the explicit connections among the many circuit analysis tools and methods.
- To develop problem-solving skills that rely on a solid conceptual foundation. This challenges students to examine many different approaches to solving a problem before writing a single equation.
- To introduce realistic engineering experiences at every opportunity. This challenges students to develop the insights of a practicing engineer and exposes them to practice of engineering.

## Why This Edition?

The Eleventh Edition of *Electric Circuits* incorporates the following new and revised elements:

- Analysis Methods – This new feature identifies the steps needed to apply a particular circuit analysis technique. Many students struggle just to get started when analyzing a circuit, and the analysis methods will reduce that struggle. Some of the analysis methods that are used most often can be found inside the book's covers for easy reference.
- Examples – Many students rely on examples when developing and refining their problem-solving skills. We identified many places in the text that needed additional examples, and as a result the number of examples has increased by nearly 35% to 200.
- End-of-chapter problems – Problem solving is fundamental to the study of circuit analysis. Having a wide variety of problems to assign and work is a key to success in any circuits course. Therefore, some existing end-of-chapter problems were revised, and some new end-of-chapter problems were added. Approximately 30% of the problems in the Eleventh Edition were rewritten.
- Fundamental equations and concepts – These important elements in the text were previously identified with margin notes. In this edition, the margin notes have been replaced by a second-color background, enlarged fonts, and a descriptive title for each fundamental equation and concept. In addition, many equation numbers have been eliminated to make it easier to distinguish fundamental equations from the many other equations in the text.
- Circuit simulation software – The PSpice® and Multisim® manuals have been revised to include screenshots from the most recent versions of these software simulation applications. Each manual presents the simulation material in the same order as the material is encountered in the text. These manuals include example simulations of circuits from the text. Icons identify end-of-chapter problems that are good candidates for simulation using either PSpice or Multisim.

- Solving simultaneous equations – Most circuit analysis techniques in this text eventually require you to solve two or more simultaneous linear algebraic equations. Appendix A has been extensively revised and includes examples of paper-and-pencil techniques, calculator techniques, and computer software techniques.
- Student workbook – Students who could benefit from additional examples and practice problems can use the Student Workbook, which has been revised for the Eleventh Edition of the text. This workbook has examples and problems covering the following material: balancing power, simple resistive circuits, node voltage method, mesh current method, Thévenin and Norton equivalents, op amp circuits, first-order circuits, second-order circuits, AC steady-state analysis, and Laplace transform circuit analysis.
- The Student Workbook now includes access to Video Solutions, complete, step-by-step solution walkthroughs to representative homework problems.
- Learning Catalytics, a “bring your own device” student engagement, assessment, and classroom intelligence system is available with the Eleventh Edition. With Learning Catalytics you can:
  - Use open-ended questions to get into the minds of students to understand what they do or don’t know and adjust lectures accordingly.
  - Use a wide variety of question types to sketch a graph, annotate a circuit diagram, compose numeric or algebraic answers, and more.
  - Access rich analytics to understand student performance.
  - Use pre-built questions or add your own to make Learning Catalytics fit your course exactly.
- Pearson Mastering Engineering is an online tutorial and assessment program that provides students with personalized feedback and hints and instructors with diagnostics to track students’ progress. With the Eleventh Edition, Mastering Engineering will offer new enhanced end-of-chapter problems with hints and feedback, Coaching Activities, and Adaptive Follow-Up assignments. Visit [www.masteringengineering.com](http://www.masteringengineering.com) for more information.

## Hallmark Features

### Analysis Methods

Students encountering circuit analysis for the first time can benefit from step-by-step directions that lead them to a problem’s solution. We have compiled these directions in a collection of analysis methods, and revised many of the examples in the text to employ these analysis methods.

### Chapter Problems

Users of *Electric Circuits* have consistently rated the Chapter Problems as one of the book’s most attractive features. In the Eleventh Edition, there are 1185 end-of-chapter problems with approximately 30% that have been revised from the previous edition. Problems are organized at the end of each chapter by section.

### Practical Perspectives

The Eleventh Edition continues using Practical Perspectives to introduce the chapter. They provide real-world circuit examples, taken from real-world devices. Every chapter begins by describing a practical application of the



material that follows. After presenting that material, the chapter revisits the Practical Perspective, performing a quantitative circuit analysis using the newly introduced chapter material. A special icon identifies end-of-chapter problems directly related to the Practical Perspective application. These problems provide additional opportunities for solving real-world problems using the chapter material.

## Assessment Problems

Each chapter begins with a set of chapter objectives. At key points in the chapter, you are asked to stop and assess your mastery of a particular objective by solving one or more assessment problems. The answers to all of the assessment problems are given at the conclusion of each problem, so you can check your work. If you are able to solve the assessment problems for a given objective, you have mastered that objective. If you need more practice, several end-of-chapter problems that relate to the objective are suggested at the conclusion of the assessment problems.

## Examples

Every chapter includes many examples that illustrate the concepts presented in the text in the form of a numeric example. There are now nearly 200 examples in this text, an increase of about 35% when compared to the previous edition. The examples illustrate the application of a particular concept, often employ an Analysis Method, and exemplify good problem-solving skills.

## Fundamental Equations and Concepts

Throughout the text, you will see fundamental equations and concepts set apart from the main text. This is done to help you focus on some of the key principles in electric circuits and to help you navigate through the important topics.

## Integration of Computer Tools

Computer tools can assist students in the learning process by providing a visual representation of a circuit's behavior, validating a calculated solution, reducing the computational burden of more complex circuits, and iterating toward a desired solution using parameter variation. This computational support is often invaluable in the design process. The Eleventh Edition supports PSpice and Multisim, both popular computer tools for circuit simulation and analysis. Chapter problems suited for exploration with PSpice and Multisim are marked accordingly.

## Design Emphasis

The Eleventh Edition continues to support the emphasis on the design of circuits in many ways. First, many of the Practical Perspective discussions focus on the design aspects of the circuits. The accompanying Chapter Problems continue the discussion of the design issues in these practical examples. Second, design-oriented Chapter Problems have been labeled explicitly, enabling students and instructors to identify those problems with a design focus. Third, the identification of problems suited to exploration with PSpice or Multisim suggests design opportunities using these software tools. Fourth, some problems in nearly every chapter focus on the use of realistic component values in achieving a desired circuit design. Once such a problem has been analyzed, the student can proceed to a laboratory to build and test the circuit, comparing the analysis with the measured performance of the actual circuit.

## Accuracy

All text and problems in the Eleventh Edition have undergone our strict hallmark accuracy checking process, to ensure the most error-free book possible.

## Resources For Students

**Mastering Engineering.** Mastering Engineering provides tutorial homework problems designed to emulate the instructor's office hour environment, guiding students through engineering concepts with self-paced individualized coaching. These in-depth tutorial homework problems provide students with feedback specific to their errors and optional hints that break problems down into simpler steps. Visit [www.masteringengineering.com](http://www.masteringengineering.com) for more information.

**Learning Catalytics.** Learning Catalytics is an interactive student response tool that encourages team-based learning by using student's smartphones, tablets, or laptops to engage them in interactive tasks and thinking. Visit [www.learningcatalytics.com](http://www.learningcatalytics.com) for more information.

**Student Workbook.** This resource teaches students techniques for solving problems presented in the text. Organized by concepts, this is a valuable problem-solving resource for all levels of students. The Student Workbook now includes access to Video Solutions, complete, step-by-step solution walkthroughs to representative homework problems.

**Introduction to Multisim and Introduction to PSpice Manuals**—Updated for the Eleventh Edition, these manuals are excellent resources for those wishing to integrate PSpice or Multisim into their classes.

## Resources for Instructors

All instructor resources are available for download at [www.pearsonhighered.com](http://www.pearsonhighered.com). If you are in need of a login and password for this site, please contact your local Pearson representative.

**Instructor Solutions Manual**—Fully worked-out solutions to Assessment Problems and end-of-chapter problems.

**PowerPoint lecture images**—All figures from the text are available in PowerPoint for your lecture needs. An additional set of full lecture slides with embedded assessment questions are available upon request.

**MasteringEngineering.** This online tutorial and assessment program allows you to integrate dynamic homework with automated grading and personalized feedback. MasteringEngineering allows you to easily track the performance of your entire class on an assignment-by-assignment basis, or the detailed work of an individual student. For more information visit [www.masteringengineering.com](http://www.masteringengineering.com).

**Learning Catalytics**—This “bring your own device” student engagement, assessment and classroom intelligence system enables you to measure student learning during class, and adjust your lectures accordingly. A wide variety of question and answer types allows you to author your own questions, or you can use questions already authored into the system. For more information visit [www.learningcatalytics.com](http://www.learningcatalytics.com) or click on the Learning Catalytics link inside Mastering Engineering.

## Prerequisites

In writing the first 12 chapters of the text, we have assumed that the reader has taken a course in elementary differential and integral calculus. We have

also assumed that the reader has had an introductory physics course, at either the high school or university level, that introduces the concepts of energy, power, electric charge, electric current, electric potential, and electromagnetic fields. In writing the final six chapters, we have assumed the student has had, or is enrolled in, an introductory course in differential equations.

## Course Options

The text has been designed for use in a one-semester, two-semester, or a three-quarter sequence.

- *Single-semester course:* After covering Chapters 1–4 and Chapters 6–10 (omitting Sections 7.7 and 8.5) the instructor can develop the desired emphasis by covering Chapter 5 (operational amplifiers), Chapter 11 (three-phase circuits), Chapters 13 and 14 (Laplace methods), or Chapter 18 (Two-Port Circuits).
- *Two-semester sequence:* Assuming three lectures per week, cover the first nine chapters during the first semester, leaving Chapters 10–18 for the second semester.
- *Academic quarter schedule:* Cover Chapters 1–6 in the first quarter, Chapters 7–12 in the second quarter, and Chapters 13–18 in the third quarter.

Note that the introduction to operational amplifier circuits in Chapter 5 can be omitted with minimal effect on the remaining material. If Chapter 5 is omitted, you should also omit Section 7.7, Section 8.5, Chapter 15, and those assessment problems and end-of-chapter problems that pertain to operational amplifiers.

There are several appendixes at the end of the book to help readers make effective use of their mathematical background. Appendix A presents several different methods for solving simultaneous linear equations; complex numbers are reviewed in Appendix B; Appendix C contains additional material on magnetically coupled coils and ideal transformers; Appendix D contains a brief discussion of the decibel; Appendix E is dedicated to Bode diagrams; Appendix F is devoted to an abbreviated table of trigonometric identities that are useful in circuit analysis; and an abbreviated table of useful integrals is given in Appendix G. Appendix H provides tables of common standard component values for resistors, inductors, and capacitors, to be used in solving many end-of-chapter problems. Selected Answers provides answers to selected end-of-chapter problems.

## Acknowledgments

I will be forever grateful to Jim Nilsson for giving me the opportunity to collaborate with him on this textbook. I started by revising the PSpice supplement for the Third Edition, and became a co-author of the Fifth Edition. Jim was a patient and gracious mentor, and I learned so much from him about teaching and writing and hard work. It is a great honor to be associated with him through this textbook, and to impact the education of the thousands of students who use this text.


There were many hard-working people behind the scenes at our publisher who deserve my thanks and gratitude for their efforts on behalf of the Eleventh Edition. At Pearson, I would like to thank Norrin Dias, Erin Ault, Rose Kernan, and Scott Disanno for their continued support and encouragement, their professional demeanor, their willingness to lend an ear, and their months of long hours and no weekends. The author would also like to



acknowledge the staff at Integra Software Solutions for their dedication and hard work in typesetting this text.

I am very grateful for the many instructors and students who have done formal reviews of the text or offered positive feedback and suggestions for improvement more informally. I am pleased to receive email from instructors and students who use the book, even when they are pointing out an error I failed to catch in the review process. I have been contacted by people who use our text from all over the world, and I thank all of you for taking the time to do so. I use as many of your suggestions as possible to continue to improve the content, the pedagogy, and the presentation in this text. I am privileged to have the opportunity to impact the educational experience of the many thousands of future engineers who will use this text.

SUSAN A. RIEDEL

 

# ELECTRIC CIRCUITS

ELEVENTH EDITION

## CHAPTER

# 1

# Circuit Variables

### CHAPTER CONTENTS

- 1.1 **Electrical Engineering: An Overview** p. 4
- 1.2 **The International System of Units** p. 9
- 1.3 **Circuit Analysis: An Overview** p. 11
- 1.4 **Voltage and Current** p. 12
- 1.5 **The Ideal Basic Circuit Element** p. 14
- 1.6 **Power and Energy** p. 15

### CHAPTER OBJECTIVES

- 1 Understand and be able to use SI units and the standard prefixes for powers of 10.
- 2 Know and be able to use the definitions of *voltage* and *current*.
- 3 Know and be able to use the definitions of *power* and *energy*.
- 4 Be able to use the passive sign convention to calculate the power for an ideal basic circuit element given its voltage and current.

**Electrical engineering** is an exciting and challenging profession for anyone who has a genuine interest in, and aptitude for, applied science and mathematics. Electrical engineers play a dominant role in developing systems that change the way people live and work. Satellite communication links, cell phones, computers, televisions, diagnostic and surgical medical equipment, robots, and aircraft represent systems that define a modern technological society. As an electrical engineer, you can participate in this ongoing technological revolution by improving and refining existing systems and by discovering and developing new systems to meet the needs of our ever-changing society.

This text introduces you to electrical engineering using the analysis and design of linear circuits. We begin by presenting an overview of electrical engineering, some ideas about an engineering point of view as it relates to circuit analysis, and a review of the International System of Units. We then describe generally what circuit analysis entails. Next, we introduce the concepts of voltage and current. We continue by discussing the ideal basic element and the need for a polarity reference system. We conclude the chapter by describing how current and voltage relate to power and energy.

# ■ Practical Perspective

## Balancing Power

One of the most important skills you will develop is the ability to check your answers for the circuits you design and analyze using the tools developed in this text. A common method used to check for valid answers is to calculate the power in the circuit. The linear circuits we study have no net power, so the sum of the power associated with all circuit components must be zero. If the total power for the circuit is zero, we say that the power balances, but if the total power is not zero, we need to find the errors in our calculation.


As an example, we will consider a simple model for distributing electricity to a typical home. (Note that a

more realistic model will be investigated in the Practical Perspective for Chapter 9.) The components labeled a and b represent the source of electrical power for the home. The components labeled c, d, and e represent the wires that carry the electrical current from the source to the devices in the home requiring electrical power. The components labeled f, g, and h represent lamps, televisions, hair dryers, refrigerators, and other devices that require power.

Once we have introduced the concepts of voltage, current, power, and energy, we will examine this circuit model in detail, and use a power balance to determine whether the results of analyzing this circuit are correct.



romakoma/Shutterstock

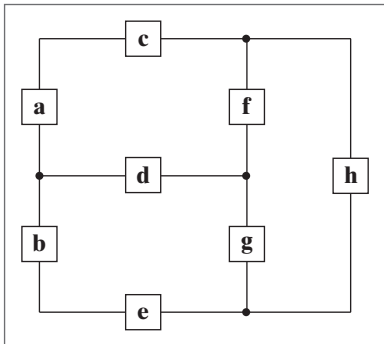

PhotoSerg/Shutterstock



AfricaStudio/Shutterstock

## 1.1 Electrical Engineering: An Overview


The electrical engineering profession focuses on systems that produce, transmit, and measure electric signals. Electrical engineering combines the physicist's models of natural phenomena with the mathematician's tools for manipulating those models to produce systems that meet practical needs. Electrical systems pervade our lives; they are found in homes, schools, workplaces, and transportation vehicles everywhere. We begin by presenting a few examples from each of the five major classifications of electrical systems:

- communication systems
- computer systems
- control systems
- power systems
- signal-processing systems

Then we describe how electrical engineers analyze and design such systems.

**Communication systems** are electrical systems that generate, transmit, and distribute information. Well-known examples include television equipment, such as cameras, transmitters, receivers, and monitors; radio telescopes, used to explore the universe; satellite systems, which return images of other planets and our own; radar systems, used to coordinate plane flights; and telephone systems.

Figure 1.1 depicts the major components of a modern telephone system that supports mobile phones, landlines, and international calling. Inside a telephone, a microphone turns sound waves into electric signals. These signals are carried to local or mobile exchanges, where they are combined with the

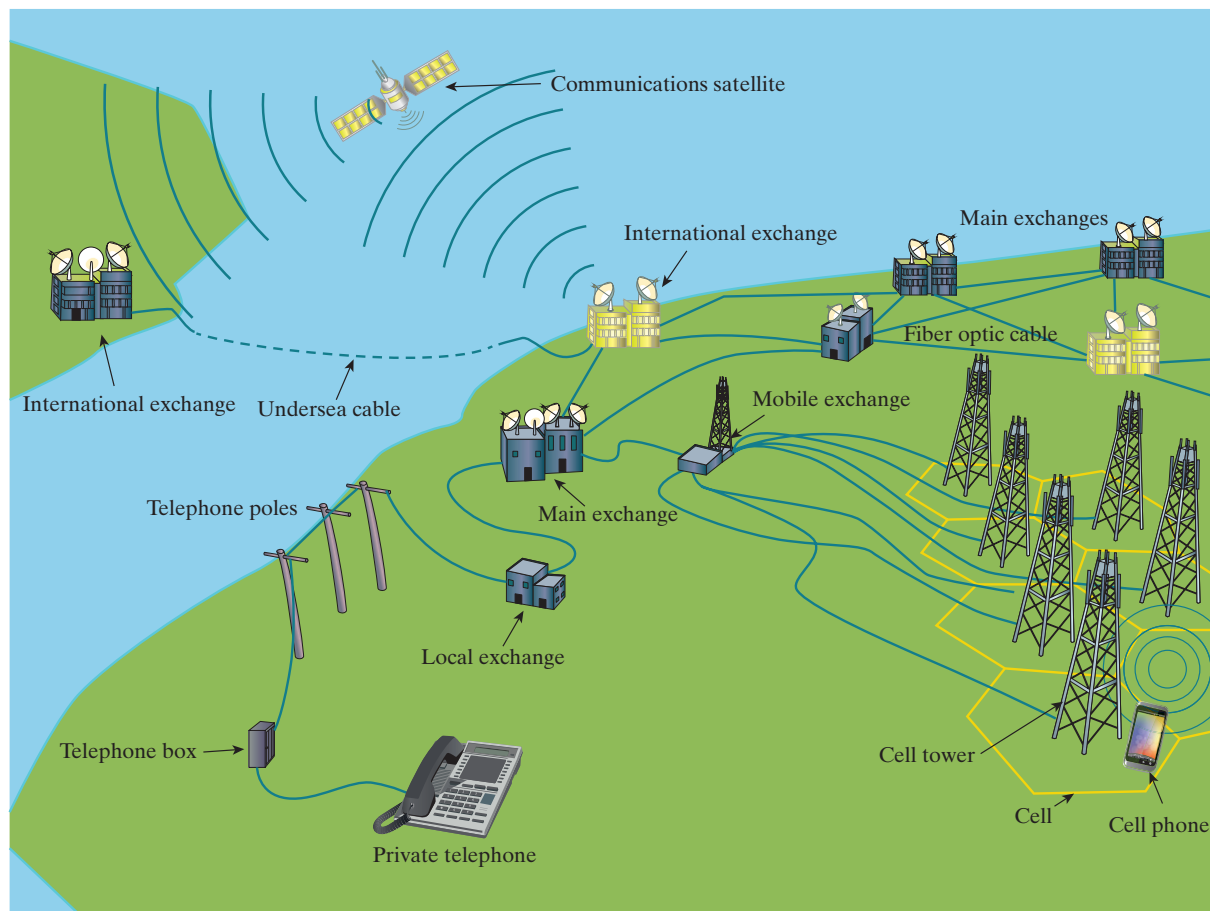

**Figure 1.1** ▲ A telephone system.

signals from tens, hundreds, or thousands of other telephones. The form of the signals can be radio waves traveling through air, electrical signals traveling in underground coaxial cable, light pulses traveling in fiber-optic cable, or microwave signals that travel through space. The combined signals are broadcast from a transmission antenna to a receiving antenna. There the combined signals are separated at an exchange, and each is routed to the appropriate telephone, where an earphone acts as a speaker to convert the received electric signals back into sound waves. At each stage of the process, electric circuits operate on the signals. Imagine the challenge involved in designing, building, and operating each circuit in a way that guarantees that all of the hundreds of thousands of simultaneous calls have high-quality connections.


**Computer systems** use electric signals to process information ranging from word processing to mathematical computations. Systems range in size and power from simple calculators to personal computers to supercomputers that perform such complex tasks as processing weather data and modeling chemical interactions of complex organic molecules. These systems include networks of integrated circuits—miniature assemblies of hundreds, thousands, or millions of electrical components that often operate at speeds and power levels close to fundamental physical limits, including the speed of light and the thermodynamic laws.

**Control systems** use electric signals to regulate processes. Examples include the control of temperatures, pressures, and flow rates in an oil refinery; the fuel–air mixture in a fuel-injected automobile engine; mechanisms such as the motors, doors, and lights in elevators; and the locks in the Panama Canal. The autopilot and autoland systems that help to fly and land airplanes are also familiar control systems.

**Power systems** generate and distribute electric power. Electric power, which is the foundation of our technology-based society, usually is generated in large quantities by nuclear, hydroelectric, solar, and thermal (coal-, oil-, or gas-fired) generators. Power is distributed by a grid of conductors that crisscross the country. A major challenge in designing and operating such a system is to provide sufficient redundancy and control so that failure of any piece of equipment does not leave a city, state, or region completely without power.

**Signal-processing systems** act on electric signals that represent information. They transform the signals and the information contained in them into a more suitable form. There are many different ways to process the signals and their information. For example, image-processing systems gather massive quantities of data from orbiting weather satellites, reduce the amount of data to a manageable level, and transform the remaining data into a video image for the evening news broadcast. A magnetic resonance imaging (MRI) scan is another example of an image-processing system. It takes signals generated by powerful magnetic fields and radio waves and transforms them into a detailed, three-dimensional image such as the one shown in Fig. 1.2, which can be used to diagnose disease and injury.

Considerable interaction takes place among the engineering disciplines involved in designing and operating these five classes of systems. Thus, communications engineers use digital computers to control the flow of information. Computers contain control systems, and control systems contain computers. Power systems require extensive communications systems to coordinate safely and reliably the operation of components, which may be spread across a continent. A signal-processing system may involve a communications link, a computer, and a control system.

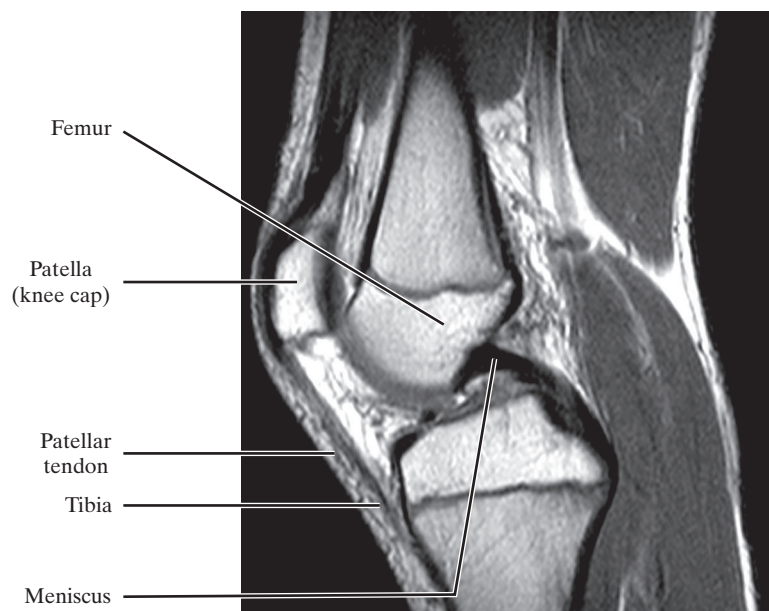


**Figure 1.2** ▲ An MRI scan of an adult knee joint.  
Neil Borden/Science Source/Getty Images



A good example of the interaction among systems is a commercial airplane, such as the one shown in Fig. 1.3. A sophisticated communications system enables the pilot and the air traffic controller to monitor the plane's location, permitting the air traffic controller to design a safe flight path for all of the nearby aircraft and enabling the pilot to keep the plane on its designated path. An onboard computer system manages engine functions, implements the navigation and flight control systems, and generates video information screens in the cockpit. A complex control system uses cockpit commands to adjust the position and speed of the airplane, producing the appropriate signals to the engines and the control surfaces (such as the wing flaps, ailerons, and rudder) to ensure the plane remains safely airborne and on the desired flight path. The plane must have its own power system to stay aloft and to provide and distribute the electric power needed to keep the cabin lights on, make the coffee, and activate the entertainment system. Signal-processing systems reduce the noise in air traffic communications and transform information about the plane's location into the more meaningful form of a video display in the cockpit. Engineering challenges abound in the design of each of these systems and their integration into a coherent whole. For example, these systems must operate in widely varying and unpredictable environmental conditions. Perhaps the most important engineering challenge is to guarantee that sufficient redundancy is incorporated in the designs, ensuring that passengers arrive safely and on time at their desired destinations.

Although electrical engineers may be interested primarily in one area, they must also be knowledgeable in other areas that interact with this area of interest. This interaction is part of what makes electrical engineering a challenging and exciting profession. The emphasis in engineering is on making things work, so an engineer is free to acquire and use any technique from any field that helps to get the job done.

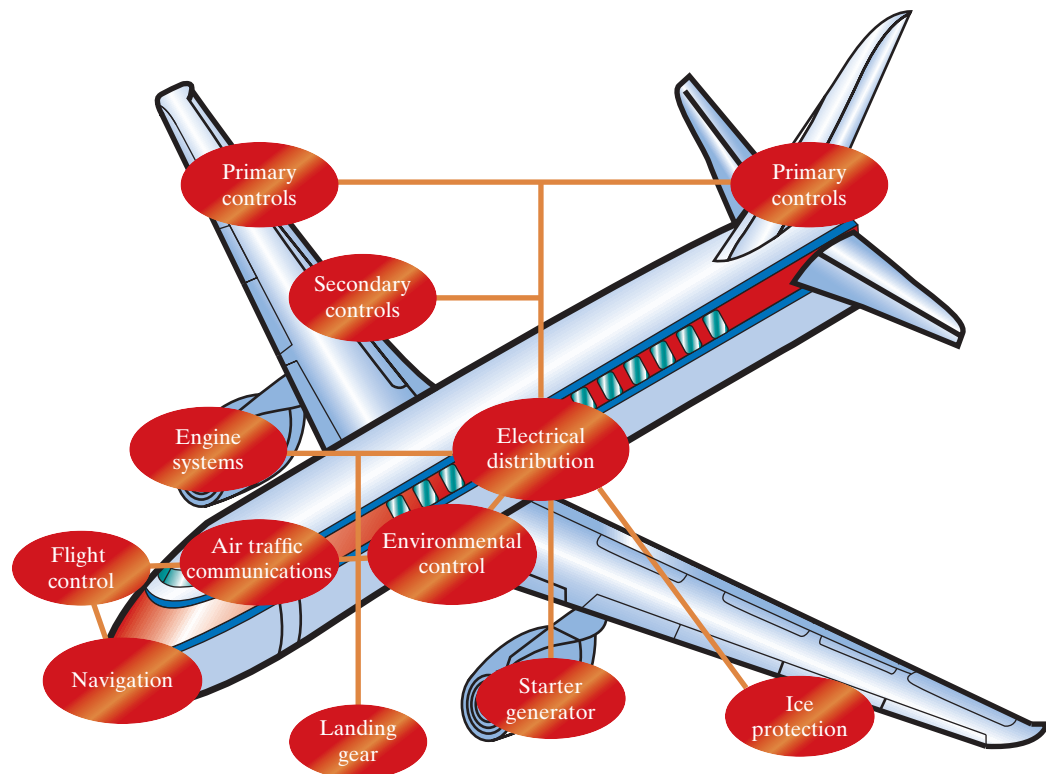

**Figure 1.3** ▲ Interacting systems on a commercial aircraft.



## Circuit Theory

An **electric circuit** is a mathematical model that approximates the behavior of an actual electrical system. Since electric circuits are found in every branch of electrical engineering, they provide an important foundation for learning how to design and operate systems such as those just described. The models, the mathematical techniques, and the language of circuit theory will form the intellectual framework for your future engineering endeavors.

Note that the term *electric circuit* is commonly used to refer to an actual electrical system as well as to the model that represents it. In this text, when we talk about an electric circuit, we always mean a model, unless otherwise stated. It is the modeling aspect of circuit theory that has broad applications across engineering disciplines.

**Circuit theory** is a special case of electromagnetic field theory: the study of static and moving electric charges. But applying generalized field theory to the study of electric signals is cumbersome and requires advanced mathematics. Consequently, a course in electromagnetic field theory is not a prerequisite to understanding the material in this book. We do, however, assume that you have had an introductory physics course in which electrical and magnetic phenomena were discussed.

Three basic assumptions permit us to use circuit theory, rather than electromagnetic field theory, to study a physical system represented by an electric circuit.

1. *Electrical effects happen instantaneously throughout a system.* We can make this assumption because we know that electric signals travel at or near the speed of light. Thus, if the system is physically small, electric signals move through it so quickly that we can consider them to affect every point in the system simultaneously. A system that is small enough so that we can make this assumption is called a **lumped-parameter system**.
2. *The net charge on every component in the system is always zero.* Thus, no component can collect a net excess of charge, although some components, as you will learn later, can hold equal but opposite separated charges.
3. *There is no magnetic coupling between the components in a system.* As we demonstrate later, magnetic coupling can occur *within* a component.

That's it; there are no other assumptions. Using circuit theory provides simple solutions (of sufficient accuracy) to problems that would become hopelessly complicated if we were to use electromagnetic field theory. These benefits are so great that engineers sometimes specifically design electrical systems to ensure that these assumptions are met. The importance of assumptions 2 and 3 becomes apparent after we introduce the basic circuit elements and the rules for analyzing interconnected elements.

Let's take a closer look at assumption 1. The question is, "How small does a physical system have to be to qualify as a lumped-parameter system?" To get a quantitative answer to this question, remember that electric signals propagate as waves. If the wavelength of the signal is large compared to the physical dimensions of the system, we have a lumped-parameter system. The wavelength  $\lambda$  is the velocity divided by the repetition rate, or **frequency**, of the signal; that is,  $\lambda = c/f$ . The frequency  $f$  is measured in hertz (Hz). For example, power systems in the United States operate at 60 Hz. If we use the speed of light ( $c = 3 \times 10^8$  m/s) as the velocity of propagation, the wavelength is  $5 \times 10^6$  m. If the power system of interest is physically smaller than this wavelength, we can represent it as a lumped-parameter system and use circuit theory to analyze its behavior.

How do we define *smaller*? A good rule is the *rule of 1/10th*: If the dimension of the system is less than 1/10th the dimension of the wavelength, you have a lumped-parameter system. Thus, as long as the physical dimension of the power system is less than  $5 \times 10^5$  m (which is about 310 miles), we can treat it as a lumped-parameter system.

Now consider a communication system that sends and receives radio signals. The propagation frequency of radio signals is on the order of  $10^9$  Hz, so the wavelength is 0.3 m. Using the rule of 1/10th, a communication system qualifies as a lumped-parameter system if its dimension is less than 3 cm. Whenever any of the pertinent physical dimensions of a system under study approaches the wavelength of its signals, we must use electromagnetic field theory to analyze that system. Throughout this book we study circuits derived from lumped-parameter systems.

## Problem Solving

As a practicing engineer, you will not be asked to solve problems that have already been solved. Whether you are improving the performance of an existing system or designing a new system, you will be working on unsolved problems. As a student, however, you will read and discuss problems with known solutions. Then, by solving related homework and exam problems on your own, you will begin to develop the skills needed to attack the unsolved problems you'll face as a practicing engineer.

Let's review several general problem-solving strategies. Many of these pertain to thinking about and organizing your solution strategy *before* proceeding with calculations.

1. *Identify what's given and what's to be found.* In problem solving, you need to know your destination before you can select a route for getting there. What is the problem asking you to solve or find? Sometimes the goal of the problem is obvious; other times you may need to paraphrase or make lists or tables of known and unknown information to see your objective.

On one hand, the problem statement may contain extraneous information that you need to weed out before proceeding. On the other hand, it may offer incomplete information or more complexities than can be handled by the solution methods you know. In that case, you'll need to make assumptions to fill in the missing information or simplify the problem context. Be prepared to circle back and reconsider supposedly extraneous information and/or your assumptions if your calculations get bogged down or produce an answer that doesn't seem to make sense.

2. *Sketch a circuit diagram or other visual model.* Translating a verbal problem description into a visual model is often a useful step in the solution process. If a circuit diagram is already provided, you may need to add information to it, such as labels, values, or reference directions. You may also want to redraw the circuit in a simpler, but equivalent, form. Later in this text you will learn the methods for developing such simplified equivalent circuits.
3. *Think of several solution methods and decide on a way of choosing among them.* This course will help you build a collection of analytical tools, several of which may work on a given problem. But one method may produce fewer equations to be solved than another, or it may require only algebra instead of calculus to reach a solution. Such efficiencies, if you can anticipate them, can streamline your calculations considerably. Having an alternative method in mind also gives you a path to pursue if your first solution attempt bogs down.

4. *Calculate a solution.* Your planning up to this point should have helped you identify a good analytical method and the correct equations for the problem. Now comes the solution of those equations. Paper-and-pencil, calculator, and computer methods are all available for performing the actual calculations of circuit analysis. Efficiency and your instructor's preferences will dictate which tools you should use.
5. *Use your creativity.* If you suspect that your answer is off base or if the calculations seem to go on and on without moving you toward a solution, you should pause and consider alternatives. You may need to revisit your assumptions or select a different solution method. Or you may need to take a less conventional problem-solving approach, such as working backward from a solution. This text provides answers to all of the Assessment Problems and many of the Chapter Problems so that you may work backward when you get stuck. In the real world, you won't be given answers in advance, but you may have a desired problem outcome in mind from which you can work backward. Other creative approaches include allowing yourself to see parallels with other types of problems you've successfully solved, following your intuition or hunches about how to proceed, and simply setting the problem aside temporarily and coming back to it later.
6. *Test your solution.* Ask yourself whether the solution you've obtained makes sense. Does the magnitude of the answer seem reasonable? Is the solution physically realizable? Are the units correct? You may want to rework the problem using an alternative method to validate your original answer and help you develop your intuition about the most efficient solution methods for various kinds of problems. In the real world, safety-critical designs are always checked by several independent means. Getting into the habit of checking your answers will benefit you both as a student and as a practicing engineer.

These problem-solving steps cannot be used as a recipe to solve every problem in this or any other course. You may need to skip, change the order of, or elaborate on certain steps to solve a particular problem. Use these steps as a guideline to develop a problem-solving style that works for you.

## 1.2 The International System of Units

Engineers use quantitative measures to compare theoretical results to experimental results and compare competing engineering designs. Modern engineering is a multidisciplinary profession in which teams of engineers work together on projects, and they can communicate their results in a meaningful way only if they all use the same units of measure. The International System of Units (abbreviated SI) is used by all the major engineering societies and most engineers throughout the world; hence we use it in this book.

The SI units are based on seven *defined* quantities:

- length
- mass
- time
- electric current
- thermodynamic temperature
- amount of substance
- luminous intensity

These quantities, along with the basic unit and symbol for each, are listed in Table 1.1. Although not strictly SI units, the familiar time units

**TABLE 1.1** The International System of Units (SI)

Quantity	Basic Unit	Symbol
Length	meter	m
Mass	kilogram	kg
Time	second	s
Electric current	ampere	A
Thermodynamic temperature	degree kelvin	K
Amount of substance	mole	mol
Luminous intensity	candela	cd

National Institute of Standards and Technology Special Publication 330, 2008 Edition, Natl. Inst. Stand. Technol. Spec. Pub. 330, 2008 Ed., 96 pages (March 2008)

of minute (60 s), hour (3600 s), and so on are often used in engineering calculations. In addition, defined quantities are combined to form **derived** units. Some quantities, such as force, energy, power, and electric charge, you already know through previous physics courses. Table 1.2 lists the derived units used in this book.

In many cases, the SI unit is either too small or too large to use conveniently. Standard prefixes corresponding to powers of 10, as listed in Table 1.3, are then applied to the basic unit. Engineers often use only the prefixes for powers divisible by 3; thus centi, deci, deka, and hecto are used rarely. Also, engineers often select the prefix that places the base number in the range between 1 and 1000. Suppose that a time calculation yields a result of  $10^{-5}$  s, that is, 0.00001 s. Most engineers would describe this quantity as 10  $\mu$ s, that is,  $10 \times 10^{-6}$  s, rather than as 0.01 ms or 10,000 ns.

Example 1.1 illustrates a method for converting from one set of units to another and also uses power-of-10 prefixes.

**TABLE 1.2** Derived Units in SI

Quantity	Unit Name (Symbol)	Formula
Frequency	hertz (Hz)	$s^{-1}$
Force	newton (N)	$kg \cdot m/s^2$
Energy or work	joule (J)	$N \cdot m$
Power	watt (W)	$J/s$
Electric charge	coulomb (C)	$A \cdot s$
Electric potential	volt (V)	$J/C$
Electric resistance	ohm ( $\Omega$ )	$V/A$
Electric conductance	siemens (S)	$A/V$
Electric capacitance	farad (F)	$C/V$
Magnetic flux	weber (Wb)	$V \cdot s$
Inductance	henry (H)	$Wb/A$

National Institute of Standards and Technology Special Publication 330, 2008 Edition, Natl. Inst. Stand. Technol. Spec. Pub. 330, 2008 Ed., 96 pages (March 2008)

**TABLE 1.3** Standardized Prefixes to Signify Powers of 10

Prefix	Symbol	Power
atto	a	$10^{-18}$
femto	f	$10^{-15}$
pico	p	$10^{-12}$
nano	n	$10^{-9}$
micro	$\mu$	$10^{-6}$
milli	m	$10^{-3}$
centi	c	$10^{-2}$
deci	d	$10^{-1}$
deka	da	10
hecto	h	$10^2$
kilo	k	$10^3$
mega	M	$10^6$
giga	G	$10^9$
tera	T	$10^{12}$

National Institute of Standards and Technology Special Publication 330, 2008 Edition, Natl. Inst. Stand. Technol. Spec. Pub. 330, 2008 Ed., 96 pages (March 2008)

**EXAMPLE 1.1** Using SI Units and Prefixes for Powers of 10

If a signal can travel in a cable at 80% of the speed of light, what length of cable, in inches, represents 1 ns?

Therefore, a signal traveling at 80% of the speed of light will cover 9.45 inches of cable in 1 nanosecond.

**Solution**

First, note that  $1 \text{ ns} = 10^{-9} \text{ s}$ . Also, recall that the speed of light  $c = 3 \times 10^8 \text{ m/s}$ . Then, 80% of the speed of light is  $0.8c = (0.8)(3 \times 10^8) = 2.4 \times 10^8 \text{ m/s}$ . Using a product of ratios, we can convert 80% of the speed of light from meters per second to inches per nanosecond. The result is the distance in inches traveled in 1 nanosecond:

$$\begin{aligned} & \frac{2.4 \times 10^8 \text{ meters}}{1 \text{ second}} \cdot \frac{1 \text{ second}}{10^9 \text{ nanoseconds}} \cdot \frac{100 \text{ centimeters}}{1 \text{ meter}} \cdot \frac{1 \text{ inch}}{2.54 \text{ centimeters}} \\ &= 9.45 \text{ inches/nanosecond.} \end{aligned}$$

**ASSESSMENT PROBLEMS**

**Objective 1**—Understand and be able to use SI units and the standard prefixes for powers of 10

**1.1** Assume a telephone signal travels through a cable at two-thirds the speed of light. How long does it take the signal to get from New York City to Miami if the distance is approximately 1100 miles?

**Answer:** 8.85 ms.

**1.2** How many dollars per millisecond would the federal government have to collect to retire a deficit of \$100 billion in one year?

**Answer:** \$3.17/ms.

*SELF-CHECK: Also try Chapter Problems 1.2, 1.3, and 1.6.*

## 1.3 Circuit Analysis: An Overview

We look broadly at engineering design, specifically the design of electric circuits, before becoming involved in the details of circuit analysis. This overview provides you with a perspective on where circuit analysis fits within the whole of circuit design. Even though this book focuses on circuit analysis, we try to provide opportunities for circuit design where appropriate.

All engineering designs begin with a need ①, as shown in Fig. 1.4. This need may come from the desire to improve on an existing design, or it may be something brand new. A careful assessment of the need results in design specifications, which are measurable characteristics of a proposed design. Once a design is proposed, the design specifications ② allow us to assess whether or not the design actually meets the need.

A concept ③ for the design comes next. The concept derives from a complete understanding of the design specifications coupled with an insight into the need, which comes from education and experience. The concept may be realized as a sketch, as a written description, or as some other form. Often the next step is to translate the concept into a mathematical model. A commonly used mathematical model for electrical systems is a circuit model ④.

The elements that make up the circuit model are called ideal circuit components. An **ideal circuit component** is a mathematical model of an actual electrical component, like a battery or a light bulb. The ideal circuit

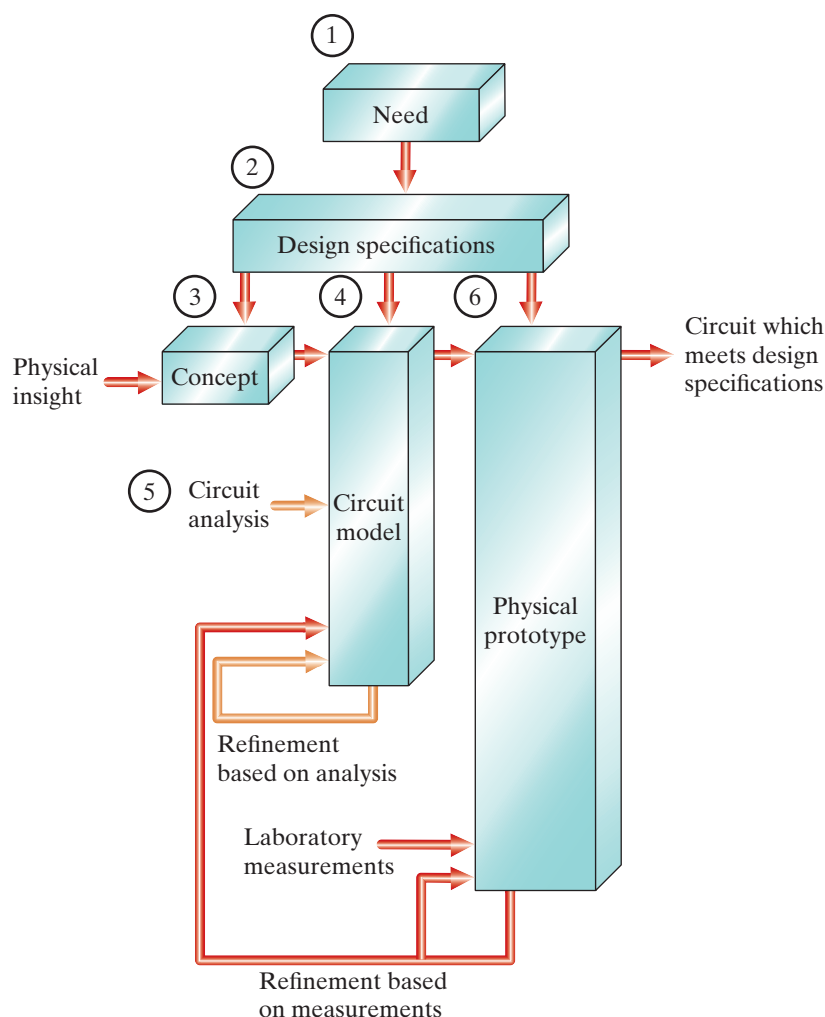


Figure 1.4 ▲ A conceptual model for electrical engineering design.

components used in a circuit model should represent the behavior of the actual electrical components to an acceptable degree of accuracy. The tools of circuit analysis (5), the focus of this book, are then applied to the circuit. **Circuit analysis** uses mathematical techniques to predict the behavior of the circuit model and its ideal circuit components. A comparison between the desired behavior, from the design specifications, and the predicted behavior, from circuit analysis, may lead to refinements in the circuit model and its ideal circuit elements. Once the desired and predicted behaviors are in agreement, a physical prototype (6) can be constructed.

The **physical prototype** is an actual electrical system, constructed from actual electrical components. Measurements determine the quantitative behavior of the physical system. This actual behavior is compared with the desired behavior from the design specifications and the predicted behavior from circuit analysis. The comparisons may result in refinements to the physical prototype, the circuit model, or both. This iterative process, in which models, components, and systems are continually refined, usually produces a design that accurately satisfies the design specifications and thus meets the need.

Circuit analysis clearly plays a very important role in the design process. Because circuit analysis is applied to circuit models, practicing engineers try to use mature circuit models so that the resulting designs will meet the design specifications in the first iteration. In this book, we use models that have been tested for at least 40 years;

you can assume that they are mature. The ability to model actual electrical systems with ideal circuit elements makes circuit theory extremely useful to engineers.

Saying that the interconnection of ideal circuit elements can be used to quantitatively predict the behavior of a system implies that we can describe the interconnection with mathematical equations. For the mathematical equations to be useful, we must write them in terms of measurable quantities. In the case of circuits, these quantities are voltage and current, which we discuss in Section 1.4. The study of circuit analysis involves understanding the behavior of each ideal circuit element in terms of its voltage and current and understanding the constraints imposed on the voltage and current as a result of interconnecting the ideal elements.

## 1.4 Voltage and Current

The concept of electric charge is the basis for describing all electrical phenomena. Let's review some important characteristics of electric charge.

- Electric charge is bipolar, meaning that electrical effects are described in terms of positive and negative charges.
- Electric charge exists in discrete quantities, which are integer multiples of the electronic charge,  $1.6022 \times 10^{-19} \text{ C}$ .
- Electrical effects are attributed to both the separation of charge and charges in motion.



In circuit theory, the separation of charge creates an electric force (voltage), and the motion of charge creates an electric fluid (current).

The concepts of voltage and current are useful from an engineering point of view because they can be expressed quantitatively. Whenever positive and negative charges are separated, energy is expended. **Voltage** is the energy per unit charge created by the separation. We express this ratio in differential form as

#### DEFINITION OF VOLTAGE

$$v = \frac{dw}{dq}, \quad (1.1)$$

where

- $v$  = the voltage in volts,
- $w$  = the energy in joules,
- $q$  = the charge in coulombs.

The electrical effects caused by charges in motion depend on the rate of charge flow. The rate of charge flow is known as the **electric current**, which is expressed as

#### DEFINITION OF CURRENT

$$i = \frac{dq}{dt}, \quad (1.2)$$

where

- $i$  = the current in amperes,
- $q$  = the charge in coulombs,
- $t$  = the time in seconds.

Equations 1.1 and 1.2 define the magnitude of voltage and current, respectively. The bipolar nature of electric charge requires that we assign polarity references to these variables. We will do so in Section 1.5.

Although current is made up of discrete moving electrons, we do not need to consider them individually because of the enormous number of them. Rather, we can think of electrons and their corresponding charge as one smoothly flowing entity. Thus,  $i$  is treated as a continuous variable.

One advantage of using *circuit models* is that we can model a component strictly in terms of the voltage and current at its terminals. Thus, two physically different components could have the same relationship between the terminal voltage and terminal current. If they do, for purposes of circuit analysis, they are identical. Once we know how a component behaves at its terminals, we can analyze its behavior in a circuit. However, when developing *component models*, we are interested in a component's internal behavior. We might want to know, for example, whether charge conduction is taking place because of free electrons moving through the crystal lattice structure of a metal or whether it is because of electrons moving within the covalent bonds of a semiconductor material. These concerns are beyond the realm of circuit theory, so in this book we use component models that have already been developed.

## 1.5 The Ideal Basic Circuit Element

An **ideal basic circuit element** has three attributes.


1. It has only two terminals, which are points of connection to other circuit components.
2. It is described mathematically in terms of current and/or voltage.
3. It cannot be subdivided into other elements.

Using the word *ideal* implies that a basic circuit element does not exist as a realizable physical component. Ideal elements can be connected in order to model actual devices and systems, as we discussed in Section 1.3. Using the word *basic* implies that the circuit element cannot be further reduced or subdivided into other elements. Thus, the basic circuit elements form the building blocks for constructing circuit models, but they themselves cannot be modeled with any other type of element.

Figure 1.5 represents an ideal basic circuit element. The box is blank because we are making no commitment at this time as to the type of circuit element it is. In Fig. 1.5, the voltage across the terminals of the box is denoted by  $v$ , and the current in the circuit element is denoted by  $i$ . The plus and minus signs indicate the polarity reference for the voltage, and the arrow placed alongside the current indicates its reference direction.

Table 1.4 interprets the voltage polarity and current direction, given positive or negative numerical values of  $v$  and  $i$ . Note that algebraically the notion of positive charge flowing in one direction is equivalent to the notion of negative charge flowing in the opposite direction.

Assigning the reference polarity for voltage and the reference direction for current is entirely arbitrary. However, once you have assigned the references, you must write all subsequent equations to agree with the chosen references. The most widely used sign convention applied to these references is called the **passive sign convention**, which we use throughout this book.

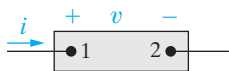

**Figure 1.5** ▲ An ideal basic circuit element.

### PASSIVE SIGN CONVENTION

Whenever the reference direction for the current in an element is in the direction of the reference voltage drop across the element (as in Fig. 1.5), use a positive sign in any expression that relates the voltage to the current. Otherwise, use a negative sign.

We apply this sign convention in all the analyses that follow. Our purpose for introducing it even before we have introduced the different types of basic circuit elements is to emphasize that selecting polarity references

**TABLE 1.4** Interpretation of Reference Directions in Fig. 1.5

Positive Value		Negative Value	
$v$	voltage drop from terminal 1 to terminal 2		voltage rise from terminal 1 to terminal 2
	or		or
	voltage rise from terminal 2 to terminal 1		voltage drop from terminal 2 to terminal 1
$i$	positive charge flowing from terminal 1 to terminal 2		positive charge flowing from terminal 2 to terminal 1
	or		or
	negative charge flowing from terminal 2 to terminal 1		negative charge flowing from terminal 1 to terminal 2



is *not* a function either of the basic elements or the type of interconnections made with the basic elements. We apply and interpret the passive sign convention for power calculations in Section 1.6.

Example 1.2 illustrates one use of the equation defining current.

### EXAMPLE 1.2 Relating Current and Charge

No charge exists at the upper terminal of the element in Fig. 1.5 for  $t < 0$ . At  $t = 0$ , a 5 A current begins to flow into the upper terminal.

- Derive the expression for the charge accumulating at the upper terminal of the element for  $t > 0$ .
- If the current is stopped after 10 seconds, how much charge has accumulated at the upper terminal?

#### Solution

- From the definition of current given in Eq. 1.2, the expression for charge accumulation due to current flow is

$$q(t) = \int_0^t i(x) dx.$$

Therefore,

$$q(t) = \int_0^t 5 dx = 5x \Big|_0^t = 5t - 5(0) = 5t \text{ C} \quad \text{for } t > 0.$$

- The total charge that accumulates at the upper terminal in 10 seconds due to a 5 A current is  $q(10) = 5(10) = 50 \text{ C}$ .

## ASSESSMENT PROBLEMS

**Objective 2—Know and be able to use the definitions of voltage and current**

- 1.3** The current at the terminals of the element in Fig. 1.5 is

$$\begin{aligned} i &= 0, & t < 0; \\ i &= 20e^{-5000t} \text{ A}, & t \geq 0. \end{aligned}$$

Calculate the total charge (in microcoulombs) entering the element at its upper terminal.

**Answer:** 4000  $\mu\text{C}$ .

- 1.4** The expression for the charge entering the upper terminal of Fig. 1.5 is

$$q = \frac{1}{\alpha^2} - \left( \frac{t}{\alpha} + \frac{1}{\alpha^2} \right) e^{-\alpha t} \text{ C}.$$

Find the maximum value of the current entering the terminal if  $\alpha = 0.03679 \text{ s}^{-1}$ .

**Answer:** 10 A.

*SELF-CHECK: Also try Chapter Problem 1.7*

## 1.6 Power and Energy

Power and energy calculations are important in circuit analysis. Although voltage and current are useful variables in the analysis and design of electrically based systems, the useful output of the system often is nonelectrical (e.g., sound emitted from a speaker or light from a light bulb), and this output is conveniently expressed in terms of power or energy. Also, all practical devices have limitations on the amount of power that they can handle. In the design process, therefore, voltage and current calculations by themselves are not sufficient to determine whether or not a design meets its specifications.

We now relate power and energy to voltage and current and at the same time use the power calculation to illustrate the passive sign convention. Recall from basic physics that power is the time rate of expending or absorbing energy. (A water pump rated 75 kW can deliver more liters per

second than one rated 7.5 kW.) Mathematically, energy per unit time is expressed in the form of a derivative, or

### DEFINITION OF POWER

$$p = \frac{dw}{dt}, \quad (1.3)$$

where

$$\begin{aligned} p &= \text{the power in watts,} \\ w &= \text{the energy in joules,} \\ t &= \text{the time in seconds.} \end{aligned}$$

Thus, 1 W is equivalent to 1 J/s.

The power associated with the flow of charge follows directly from the definition of voltage and current in Eqs. 1.1 and 1.2, or

$$p = \frac{dw}{dt} = \left( \frac{dw}{dq} \right) \left( \frac{dq}{dt} \right),$$

so

### POWER EQUATION

$$p = vi, \quad (1.4)$$

where

$$\begin{aligned} p &= \text{the power in watts,} \\ v &= \text{the voltage in volts,} \\ i &= \text{the current in amperes.} \end{aligned}$$

Equation 1.4 shows that the **power** associated with a basic circuit element is the product of the current in the element and the voltage across the element. Therefore, power is a quantity associated with a circuit element, and we have to determine from our calculation whether power is being delivered to the circuit element or extracted from it. This information comes from correctly applying and interpreting the passive sign convention (Section 1.5).

If we use the passive sign convention, Eq. 1.4 is correct if the reference direction for the current is in the direction of the reference voltage drop across the terminals. Otherwise, Eq. 1.4 must be written with a minus sign. In other words, if the current reference is in the direction of a reference voltage rise across the terminals, the expression for the power is


$$p = -vi.$$

The algebraic sign of power is based on charge movement through voltage drops and rises. As positive charges move through a drop in voltage, they lose energy, and as they move through a rise in voltage, they gain energy. Figure 1.6 summarizes the relationship between the polarity references for voltage and current and the expression for power.

We can now state the rule for interpreting the algebraic sign of power:

### INTERPRETING ALGEBRAIC SIGN OF POWER

- If the power is positive (that is, if  $p > 0$ ), power is being delivered to the circuit element represented by the box.
- If the power is negative (that is, if  $p < 0$ ), power is being extracted from the circuit element.

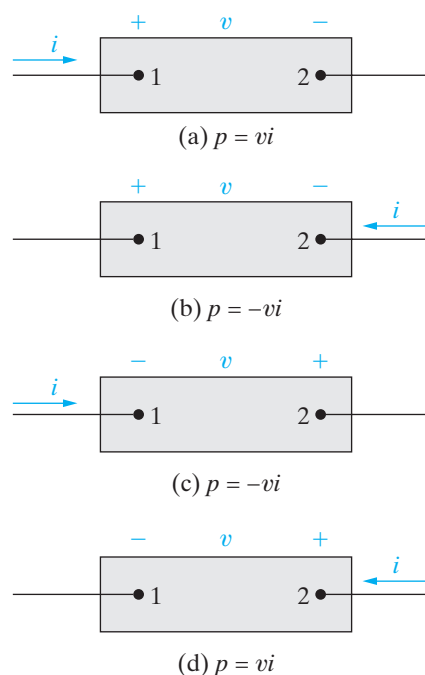

**Figure 1.6** ▲ Polarity references and the expression for power.

Example 1.3 shows that the passive sign convention generates the correct sign for power regardless of the voltage polarity and current direction you choose.

### EXAMPLE 1.3 Using the Passive Sign Convention

- a) Suppose you have selected the polarity references shown in Fig. 1.6(b). Your calculations for the current and voltage yield the following numerical results:

$$i = 4 \text{ A} \quad \text{and} \quad v = -10 \text{ V}.$$

Calculate the power associated with the circuit element and determine whether it is absorbing or supplying power.

- b) Your classmate is solving the same problem but has chosen the reference polarities shown in Fig. 1.6(c). Her calculations for the current and voltage show that

$$i = -4 \text{ A} \quad \text{and} \quad v = 10 \text{ V}.$$

What power does she calculate?

### Solution

- a) The power associated with the circuit element in Fig. 1.6(b) is

$$p = -(-10)(4) = 40 \text{ W}.$$

Thus, the circuit element is absorbing 40 W.

- b) Your classmate calculates that the power associated with the circuit element in Fig. 1.6(c) is

$$p = -(10)(-4) = 40 \text{ W}.$$

Using the reference system in Fig. 1.6(c) gives the same conclusion as using the reference system in Fig. 1.6(b)—namely, that the circuit element is absorbing 40 W. In fact, any of the reference systems in Fig. 1.6 yields this same result.

Example 1.4 illustrates the relationship between voltage, current, power, and energy for an ideal basic circuit element and the use of the passive sign convention.

### EXAMPLE 1.4 Relating Voltage, Current, Power, and Energy

Assume that the voltage at the terminals of the element in Fig. 1.5, whose current was defined in Assessment Problem 1.3, is

$$v = 0 \quad t < 0;$$

$$v = 10e^{-5000t} \text{ kV}, \quad t \geq 0.$$

- a) Calculate the power supplied to the element at 1 ms.  
b) Calculate the total energy (in joules) delivered to the circuit element.

### Solution

- a) Since the current is entering the + terminal of the voltage drop defined for the element in Fig. 1.5, we use a “+” sign in the power equation.

$$p = vi = (10,000e^{-5000t})(20e^{-5000t}) = 200,000e^{-10,000t} \text{ W}.$$

$$p(0.001) = 200,000e^{-10,000(0.001)} = 200,000e^{-10}$$

$$= 200,000(45.4 \times 10^{-6}) = 9.08 \text{ W}.$$

- b) From the definition of power given in Eq. 1.3, the expression for energy is

$$w(t) = \int_0^t p(x) dx.$$

To find the total energy delivered, integrate the expression for power from zero to infinity. Therefore,

$$w_{\text{total}} = \int_0^{\infty} 200,000e^{-10,000x} dx = \left. \frac{200,000e^{-10,000x}}{-10,000} \right|_0^{\infty}$$

$$= -20e^{-\infty} - (-20e^{-0}) = 0 + 20 = 20 \text{ J}.$$

Thus, the total energy supplied to the circuit element is 20 J.

## ASSESSMENT PROBLEMS

**Objective 3—**Know and use the definitions of *power* and *energy*; **Objective 4—**Be able to use the passive sign convention

- 1.5** Assume that a 20 V voltage drop occurs across an element from terminal 2 to terminal 1 and that a current of 4 A enters terminal 2.
- Specify the values of  $v$  and  $i$  for the polarity references shown in Fig. 1.6(a)–(d).
  - Calculate the power associated with the circuit element.
  - Is the circuit element absorbing or delivering power?

**Answer:** (a) Circuit 1.6(a):  $v = -20$  V,  $i = -4$  A;  
 circuit 1.6(b):  $v = -20$  V,  $i = 4$  A;  
 circuit 1.6(c):  $v = 20$  V,  $i = -4$  A;  
 circuit 1.6(d):  $v = 20$  V,  $i = 4$  A;  
 (b) 80 W;  
 (c) absorbing.

- 1.6** The voltage and current at the terminals of the circuit element in Fig. 1.5 are zero for  $t < 0$ . For  $t \geq 0$ , they are


$$v = 80,000te^{-500t} \text{ V}, \quad t \geq 0;$$

$$i = 15te^{-500t} \text{ A}, \quad t \geq 0.$$

- Find the time when the power delivered to the circuit element is maximum.
- Find the maximum value of power.
- Find the total energy delivered to the circuit element.

**Answer:** (a) 2 ms; (b) 649.6 mW; (c) 2.4 mJ.

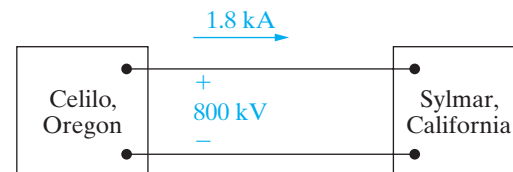- 1.7** A high-voltage direct-current (dc) transmission line between Celilo, Oregon, and Sylmar, California, is operating at 800 kV and carrying 1800 A, as shown. Calculate the power (in megawatts) at the Oregon end of the line and state the direction of power flow.




**Answer:** 1440 MW, Celilo to Sylmar

**SELF-CHECK:** Also try Chapter Problems 1.15, 1.18, and 1.25.

## Practical Perspective

### Balancing Power

A circuit model for distributing power to a typical home is shown in Fig. 1.7, with voltage polarities and current directions defined for all of the circuit components. Circuit analysis gives values for all of these voltages and currents, as summarized in Table 1.5. To determine whether or not the values given are correct, calculate the power associated with each component. Use the passive sign convention in the power calculations, as shown in the following.

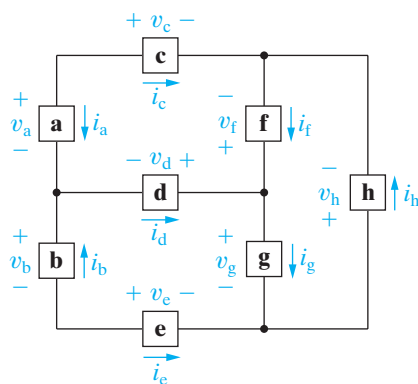

**Figure 1.7** ▲ Circuit model for power distribution in a home, with voltages and currents defined.

$$\begin{aligned} p_a &= v_a i_a = (120)(-10) = -1200 \text{ W} & p_b &= -v_b i_b = -(120)(9) = -1080 \text{ W} \\ p_c &= v_c i_c = (10)(10) = 100 \text{ W} & p_d &= -v_d i_d = -(10)(1) = -10 \text{ W} \\ p_e &= v_e i_e = (-10)(-9) = 90 \text{ W} & p_f &= -v_f i_f = -(-100)(5) = 500 \text{ W} \\ p_g &= v_g i_g = (120)(4) = 480 \text{ W} & p_h &= v_h i_h = (-220)(-5) = 1100 \text{ W} \end{aligned}$$

The power calculations show that components a, b, and d are supplying power, since the power values are negative, while components

c, e, f, g, and h are absorbing power. Now check to see if the power balances by finding the total power supplied and the total power absorbed.

$$\begin{aligned} p_{\text{supplied}} &= p_a + p_b + p_d = -1200 - 1080 - 10 = -2290 \text{ W} \\ p_{\text{absorbed}} &= p_c + p_e + p_f + p_g + p_h \\ &= 100 + 90 + 500 + 480 + 1100 = 2270 \text{ W} \\ p_{\text{supplied}} + p_{\text{absorbed}} &= -2290 + 2270 = -20 \text{ W} \end{aligned}$$

Something is wrong—if the values for voltage and current in this circuit are correct, the total power should be zero! There is an error in the data, and we can find it from the calculated powers if the error exists in the sign of a single component. Note that if we divide the total power by 2, we get  $-10 \text{ W}$ , which is the power calculated for component d. If the power for component d is  $+10 \text{ W}$ , the total power would be 0. Circuit analysis techniques from upcoming chapters can be used to show that the current through component d should be  $-1 \text{ A}$ , not  $+1 \text{ A}$  as given in Table 1.5.

*SELF-CHECK: Assess your understanding of the Practical Perspective by trying Chapter Problems 1.34 and 1.35.*

TABLE 1.5 Voltage and Current Values for the Circuit in Fig. 1.7		
Component	$v(\text{V})$	$i(\text{A})$
a	120	$-10$
b	120	9
c	10	10
d	10	1
e	$-10$	$-9$
f	$-100$	5
g	120	4
h	$-220$	$-5$

## Summary

- The International System of Units (SI) enables engineers to communicate in a meaningful way about quantitative results. Table 1.1 summarizes the SI units; Table 1.2 presents some useful derived SI units. (See page 10.)
- A circuit model is a mathematical representation of an electrical system. Circuit analysis, used to predict the behavior of a circuit model, is based on the variables of voltage and current. (See page 12.)
- **Voltage** is the energy per unit charge created by charge separation and has the SI unit of volt. (See page 13.)

$$v = dw/dq$$

- **Current** is the rate of charge flow and has the SI unit of ampere. (See page 13.)
- The **ideal basic circuit element** is a two-terminal component that cannot be subdivided; it can be described

$$i = dq/dt$$

mathematically in terms of its terminal voltage and current. (See page 14.)

- The **passive sign convention** uses a positive sign in the expression that relates the voltage and current at the terminals of an element when the reference direction for the current through the element is in the direction of the reference voltage drop across the element. (See page 14.)
- **Power** is energy per unit of time and is equal to the product of the terminal voltage and current; it has the SI unit of watt. (See page 16.)

$$p = dw/dt = vi$$

The algebraic sign of power is interpreted as follows:

- If  $p > 0$ , power is being delivered to the circuit or circuit component.
- If  $p < 0$ , power is being extracted from the circuit or circuit component. (See page 16.)

## Problems

### Section 1.2

- 1.1** The line described in Assessment Problem 1.7 is 845 mi in length. The line contains four conductors, each weighing 2526 lb per 1000 ft. How many kilograms of conductor are in the line?
- 1.2** A 32-inch monitor contains  $3840 \times 2160$  picture elements, or pixels. Each pixel is represented in 24 bits of memory. A byte of memory is 8 bits.
- How many megabytes (MB) of memory are required to store the information displayed on the monitor?
  - To display a video on the monitor, the image must be refreshed 30 times per second. How many terabytes (TB) of memory are required to store a 2 hr video?
  - For the video described in part (b), how fast must the image data in memory be moved to the monitor? Express your answer in gigabits per second (Gb/s).
- 1.3** Some species of bamboo can grow (250 mm/day). Assume individual cells in the plant are  $10 \mu\text{m}$  long.
- How long, on average, does it take a bamboo stalk to grow 1 cell length?
  - How many cell lengths are added in one week, on average?
- 1.4** A hand-held video player displays  $480 \times 320$  picture elements (pixels) in each frame of the video. Each pixel requires 2 bytes of memory. Videos are displayed at a rate of 30 frames per second. How many hours of video will fit in a 32 gigabyte memory?
- 1.5** The 16 gigabyte ( $\text{GB} = 2^{30}$  bytes) flash memory chip for an MP3 player is 11 mm by 15 mm by 1 mm. This memory chip holds 20,000 photos.
- How many photos fit into a cube whose sides are 1 mm?
  - How many bytes of memory are stored in a cube whose sides are  $200 \mu\text{m}$ ?
- 1.6** There are approximately 260 million passenger vehicles registered in the United States. Assume that the battery in the average vehicle stores 540 watt-hours (Wh) of energy. Estimate (in gigawatt-hours) the total energy stored in US passenger vehicles.

### Section 1.4

- 1.7** The current entering the upper terminal of Fig. 1.5 is

$$i = 24 \cos 4000t \text{ A}$$

Assume the charge at the upper terminal is zero at the instant the current is passing through its maximum value. Find the expression for  $q(t)$ .


- 1.8** How much energy is imparted to an electron as it flows through a 6 V battery from the positive to the negative terminal? Express your answer in attojoules.
- 1.9** In electronic circuits it is not unusual to encounter currents in the microampere range. Assume a  $35 \mu\text{A}$  current, due to the flow of electrons. What is the average number of electrons per second that flow past a fixed reference cross section that is perpendicular to the direction of flow?
- 1.10** There is no charge at the upper terminal of the element in Fig. 1.5 for  $t < 0$ . At  $t = 0$  a current of  $125e^{-2500t}$  mA enters the upper terminal.
- Derive the expression for the charge that accumulates at the upper terminal for  $t > 0$ .
  - Find the total charge that accumulates at the upper terminal.
  - If the current is stopped at  $t = 0.5$  ms, how much charge has accumulated at the upper terminal?
- 1.11** The current at the terminals of the element in Fig. 1.5 is
- $$i = 0, \quad t < 0;$$
- $$i = 40te^{-500t} \text{ A}, \quad t \geq 0.$$
- Find the expression for the charge accumulating at the upper terminal.
  - Find the charge that has accumulated at  $t = 1$  ms.

### Sections 1.5–1.6

- 1.12** When a car has a dead battery, it can often be started by connecting the battery from another car across its terminals. The positive terminals are connected together as are the negative terminals. The connection is illustrated in Fig. P1.12. Assume the current  $i$  in Fig. P1.12 is measured and found to be 40 A.
- Which car has the dead battery?
  - If this connection is maintained for 1.5 min, how much energy is transferred to the dead battery?




Figure P1.12

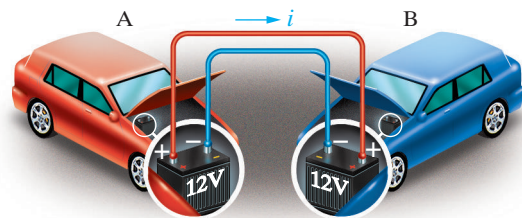

- 1.13** Two electric circuits, represented by boxes A and B, are connected as shown in Fig. P1.13. The reference direction for the current  $i$  in the interconnection and the reference polarity for the voltage  $v$  across the interconnection are as shown in the figure. For each of the following sets of numerical values, calculate the power in the interconnection and state whether the power is flowing from A to B or vice versa.

- $i = 6 \text{ A}$ ,  $v = 30 \text{ V}$
- $i = -8 \text{ A}$ ,  $v = -20 \text{ V}$
- $i = 4 \text{ A}$ ,  $v = -60 \text{ V}$
- $i = -9 \text{ A}$ ,  $v = 40 \text{ V}$

Figure P1.13

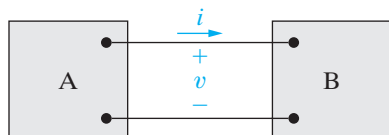

- 1.14** One 12 V battery supplies 100 mA to a boom box. How much energy does the battery supply in 4 h?
- 1.15** The references for the voltage and current at the terminals of a circuit element are as shown in Fig. 1.6(d). The numerical values for  $v$  and  $i$  are  $-20 \text{ V}$  and  $5 \text{ A}$ .
- Calculate the power at the terminals and state whether the power is being absorbed or delivered by the element in the box.
  - Given that the current is due to electron flow, state whether the electrons are entering or leaving terminal 2.
  - Do the electrons gain or lose energy as they pass through the element in the box?

- 1.16** Repeat Problem 1.15 with a current of  $-5 \text{ A}$ .

- 1.17** The manufacturer of a 6 V dry-cell flashlight battery says that the battery will deliver 15 mA for 60 continuous hours. During that time the voltage will drop from 6 V to 4 V. Assume the drop in voltage is linear with time. How much energy does the battery deliver in this 60 h interval?

- 1.18** The voltage and current at the terminals of the circuit element in Fig. 1.5 are zero for  $t < 0$ . For  $t \geq 0$  they are

$$v = 75 - 75e^{-1000t} \text{ V},$$

$$i = 50e^{-1000t} \text{ mA}.$$

- Find the maximum value of the power delivered to the circuit.
- Find the total energy delivered to the element.

- 1.19** The voltage and current at the terminals of the circuit element in Fig. 1.5 are zero for  $t < 0$ . For  $t \geq 0$  they are

$$v = 15e^{-250t} \text{ V},$$

$$i = 40e^{-250t} \text{ mA}.$$

- Calculate the power supplied to the element at 10 ms.
- Calculate the total energy delivered to the circuit element.

- 1.20** The voltage and current at the terminals of the circuit element in Fig. 1.5 are zero for  $t < 0$ . For  $t \geq 0$  they are

$$v = (1500t + 1)e^{-750t} \text{ V}, \quad t \geq 0;$$

$$i = 40e^{-750t} \text{ mA}, \quad t \geq 0.$$

- Find the time when the power delivered to the circuit element is maximum.
- Find the maximum value of  $p$  in milliwatts.
- Find the total energy delivered to the circuit element in microjoules.

- 1.21** The voltage and current at the terminals of the circuit element in Fig. 1.5 are zero for  $t < 0$ . For  $t \geq 0$  they are

$$v = 50e^{-1600t} - 50e^{-400t} \text{ V},$$

$$i = 5e^{-1600t} - 5e^{-400t} \text{ mA}.$$

- Find the power at  $t = 625 \mu\text{s}$ .
- How much energy is delivered to the circuit element between 0 and  $625 \mu\text{s}$ ?
- Find the total energy delivered to the element.



**1.22** The voltage and current at the terminals of the circuit element in Fig. 1.5 are zero for  $t < 0$ . For  $t \geq 0$  they are

PSPICE  
MULTISIM

$$v = (10,000t + 5)e^{-400t} \text{ V},$$

$$i = (40t + 0.05)e^{-400t} \text{ A}.$$

- At what instant of time is maximum power delivered to the element?
- Find the maximum power in watts.
- Find the total energy delivered to the element in microjoules.

**1.23** The voltage and current at the terminals of the circuit element in Fig. 1.5 are zero for  $t < 0$  and  $t > 40$  s. In the interval between 0 and 40 s the expressions are

PSPICE  
MULTISIM

$$v = t(1 - 0.025t) \text{ V}, \quad 0 < t < 40 \text{ s};$$

$$i = 4 - 0.2t \text{ A}, \quad 0 < t < 40 \text{ s}.$$

- At what instant of time is the power being delivered to the circuit element maximum?
- What is the power at the time found in part (a)?
- At what instant of time is the power being extracted from the circuit element maximum?
- What is the power at the time found in part (c)?
- Calculate the net energy delivered to the circuit at 0, 10, 20, 30 and 40 s.

**1.24** The voltage and current at the terminals of the element in Fig. 1.5 are

PSPICE  
MULTISIM

$$v = 250 \cos 800\pi t \text{ V}, \quad i = 8 \sin 800\pi t \text{ A}.$$

- Find the maximum value of the power being delivered to the element.
- Find the maximum value of the power being extracted from the element.
- Find the average value of  $p$  in the interval  $0 \leq t \leq 2.5$  ms.
- Find the average value of  $p$  in the interval  $0 \leq t \leq 15.625$  ms.

**1.25** The voltage and current at the terminals of the circuit element in Fig. 1.5 are zero for  $t < 0$ . For  $t \geq 0$  they are

PSPICE  
MULTISIM

$$v = 100e^{-50t} \sin 150t \text{ V},$$

$$i = 20e^{-50t} \sin 150t \text{ A}.$$

- Find the power absorbed by the element at  $t = 20$  ms.
- Find the total energy absorbed by the element.

**1.26** An industrial battery is charged over a period of several hours at a constant voltage of 120 V. Initially, the current is 10 mA and increases linearly to 15 mA in 10 ks. From 10 ks to 20 ks, the current is constant at 15 mA. From 20 ks to 30 ks the current decreases linearly to 10 mA. At 30 ks the power is disconnected from the battery.


- Sketch the current from  $t = 0$  to  $t = 30$  ks.
- Sketch the power delivered to the battery from  $t = 0$  to  $t = 30$  ks.
- Using the sketch of the power, find the total energy delivered to the battery.

**1.27** The voltage and current at the terminals of an automobile battery during a charge cycle are shown in Fig. P1.27.

PSPICE  
MULTISIM

- Calculate the total charge transferred to the battery.
- Calculate the total energy transferred to the battery.



Figure P1.27

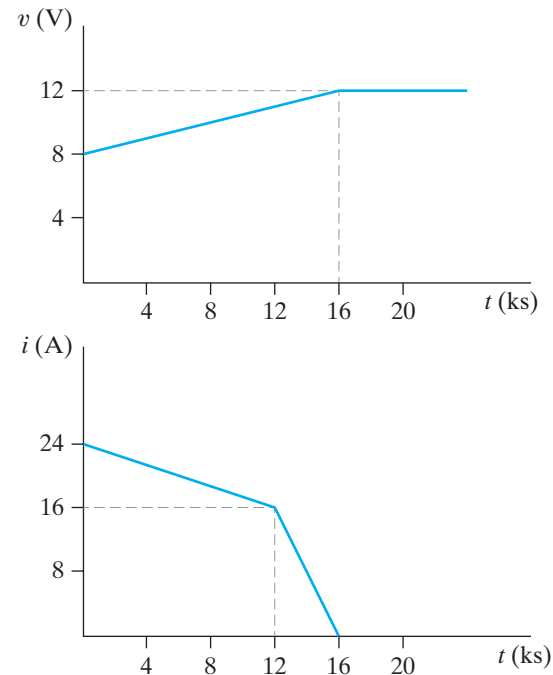

**1.28** The voltage and current at the terminals of the circuit element in Fig. 1.5 are shown in Fig. P1.28.

- Sketch the power versus  $t$  plot for  $0 \leq t \leq 50$  s.
- Calculate the energy delivered to the circuit element at  $t = 4, 12, 36,$  and  $50$  s.

Figure P1.28

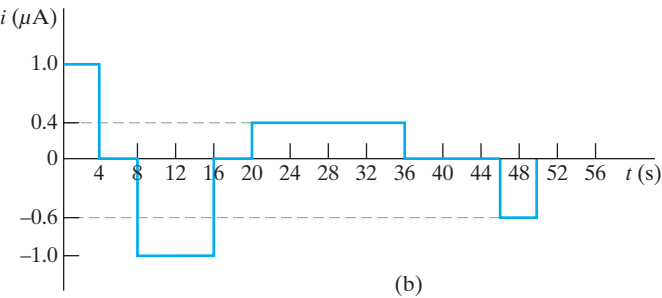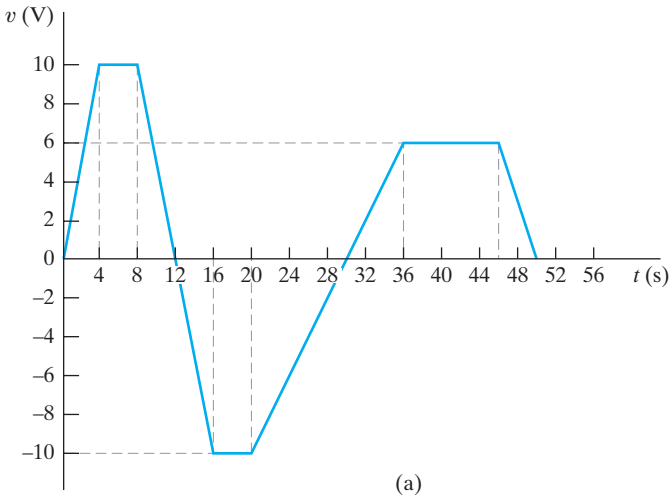

1.29 The numerical values for the currents and voltages in the circuit in Fig. P1.29 are given in Table P1.29. Find the total power developed in the circuit.

Figure P1.29

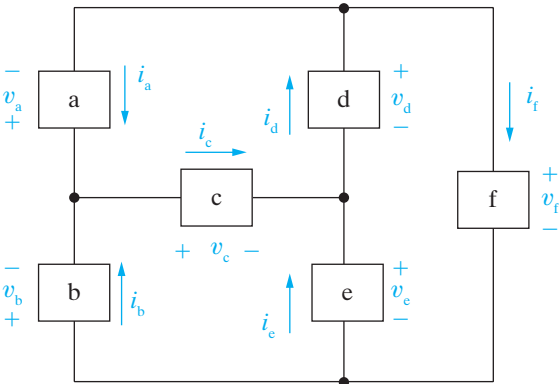


TABLE P1.29

Element	Voltage (V)	Current (mA)
a	-18	-51
b	-18	45
c	2	-6
d	20	-20
e	16	-14
f	36	31

1.30 The voltage and power values for each of the elements shown in Fig. P1.30 are given in Table P1.30.

- a) Show that the interconnection of the elements satisfies the power check.
- b) Find the value of the current through each of the elements using the values of power and voltage and the current directions shown in the figure.

Figure P1.30

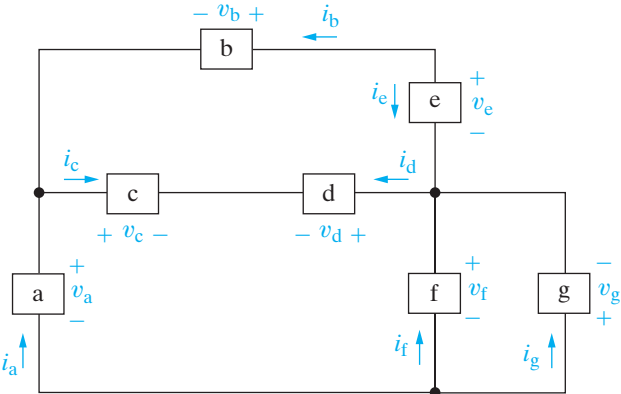


TABLE P1.30

Element	Power (kW)	Voltage (V)
a	0.6 supplied	400
b	0.05 supplied	-100
c	0.4 absorbed	200
d	0.6 supplied	300
e	0.1 absorbed	-200
f	2.0 absorbed	500
g	1.25 supplied	-500

**1.31** The numerical values of the voltages and currents in the interconnection seen in Fig. P1.31 are given in Table P1.31. Does the interconnection satisfy the power check?

Figure P1.31

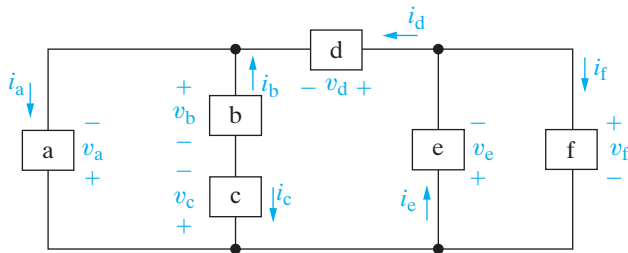


TABLE P1.31

Element	Voltage (kV)	Current (mA)
a	-3	-250
b	4	-400
c	1	400
d	1	150
e	-4	200
f	4	50

**1.32** The current and power for each of the interconnected elements in Fig. P1.32 is measured. The values are listed in Table P1.32.

- Show that the interconnection satisfies the power check.
- Identify the elements that absorb power.
- Find the voltage for each of the elements in the interconnection, using the values of power and current and the voltage polarities shown in the figure.

Figure P1.32

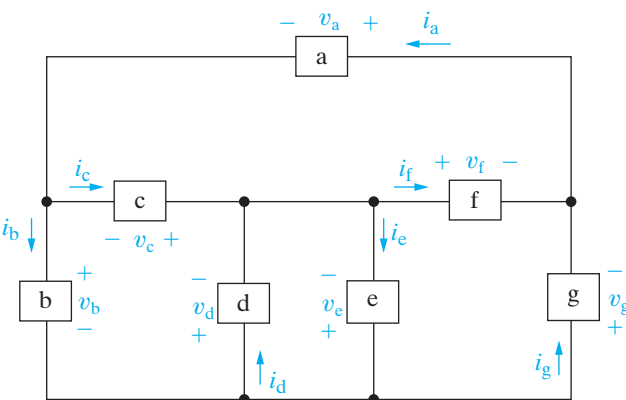


TABLE P1.32

Element	Power (mW)	Current (mA)
a	175	25
b	375	75
c	150	-50
d	-320	40
e	160	20
f	120	-30
g	-660	55

**1.33** Assume you are an engineer in charge of a project and one of your subordinate engineers reports that the interconnection in Fig. P1.33 does not pass the power check. The data for the interconnection are given in Table P1.33.

- Is the subordinate correct? Explain your answer.
- If the subordinate is correct, can you find the error in the data?

Figure P1.33

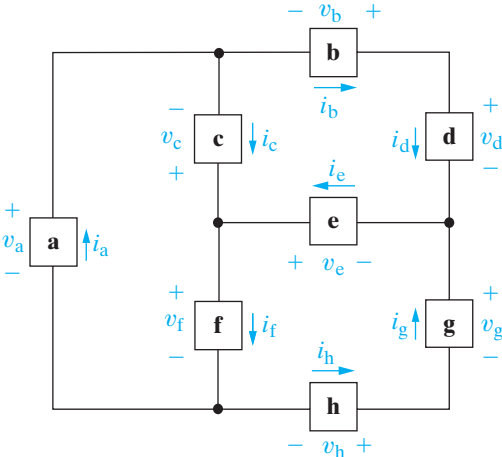


TABLE P1.33

Element	Voltage (V)	Current (A)
a	900	-22.5
b	105	-52.5
c	-600	-30.0
d	585	-52.5
e	-120	30.0
f	300	60.0
g	585	82.5
h	-165	82.5

**1.34** Show that the power balances for the circuit shown in Fig. 1.7, using the voltage and current values given in Table 1.5, with the value of the current for component d changed to  $-1$  A.

**1.35** Suppose there is no power lost in the wires used to distribute power in a typical home.

- a) Create a new model for the power distribution circuit by modifying the circuit shown in Fig 1.7. Use the same names, voltage polarities, and current directions for the components that remain in this modified model.

- b) The following voltages and currents are calculated for the components:

$$v_a = 120 \text{ V} \qquad i_a = -10 \text{ A}$$

$$v_b = 120 \text{ V} \qquad i_b = 10 \text{ A}$$

$$v_f = -120 \text{ V} \qquad i_f = 3 \text{ A}$$

$$v_g = 120 \text{ V}$$

$$v_h = -240 \text{ V} \qquad i_h = -7 \text{ A}$$

If the power in this modified model balances, what is the value of the current in component g?

# CHAPTER 2

## CHAPTER CONTENTS

- 2.1 **Voltage and Current Sources** *p. 28*
- 2.2 **Electrical Resistance (Ohm's Law)** *p. 32*
- 2.3 **Constructing a Circuit Model** *p. 36*
- 2.4 **Kirchhoff's Laws** *p. 39*
- 2.5 **Analyzing a Circuit Containing Dependent Sources** *p. 45*

## CHAPTER OBJECTIVES

- 1 Understand the symbols for and the behavior of the following ideal basic circuit elements: independent voltage and current sources, dependent voltage and current sources, and resistors.
- 2 Be able to state Ohm's law, Kirchhoff's current law, and Kirchhoff's voltage law, and be able to use these laws to analyze simple circuits.
- 3 Know how to calculate the power for each element in a simple circuit and be able to determine whether or not the power balances for the whole circuit.

## Circuit Elements

There are five ideal basic circuit elements:

- voltage sources
- current sources
- resistors
- inductors
- capacitors

In this chapter, we discuss the characteristics of the first three circuit elements—voltage sources, current sources, and resistors. Although this may seem like a small number of elements, many practical systems can be modeled with just sources and resistors. They are also a useful starting point because of their relative simplicity; the mathematical relationships between voltage and current in sources and resistors are algebraic. Thus, you will be able to begin learning the basic techniques of circuit analysis with only algebraic manipulations.


We will postpone introducing inductors and capacitors until Chapter 6, because their use requires that you solve integral and differential equations. However, the basic analytical techniques for solving circuits with inductors and capacitors are the same as those introduced in this chapter. So, by the time you need to begin manipulating more difficult equations, you should be very familiar with the methods of writing them.

## ■ Practical Perspective


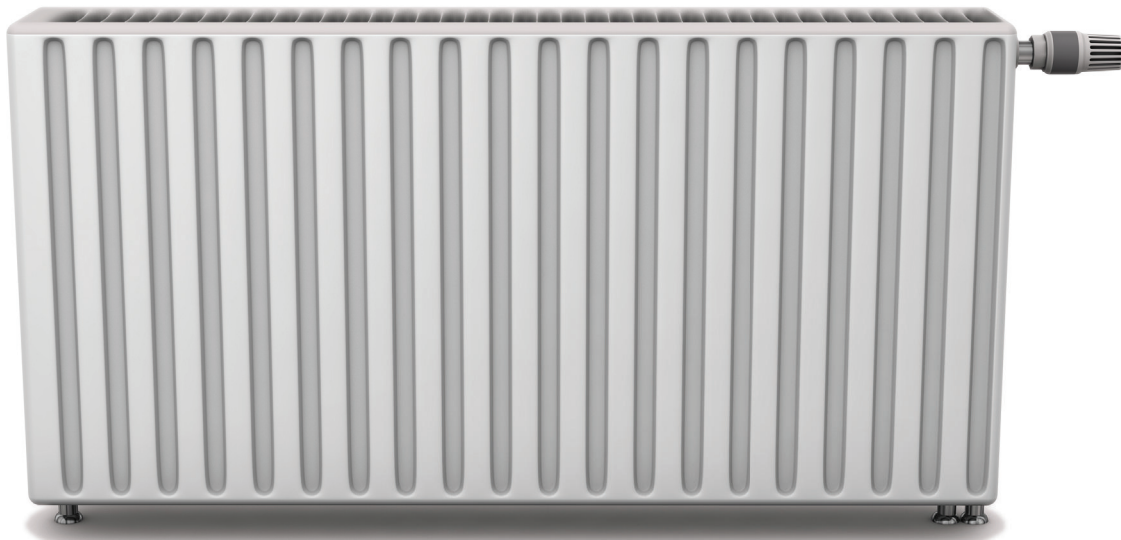
### Heating with Electric Radiators

You want to heat your small garage using a couple of electric radiators. The power and voltage requirements for each radiator are 1200 W, 240 V. But you are not sure how to wire the radiators to the power supplied to the garage. Should you use the wiring diagram on the left or the one on the right? Does it make any difference?

Once you have studied the material in this chapter, you will be able to answer these questions and determine how to heat the garage. The Practical Perspective at the end of this chapter guides you through the analysis of two circuits based on the two wiring diagrams shown below.



Style-Photography/Fotolia

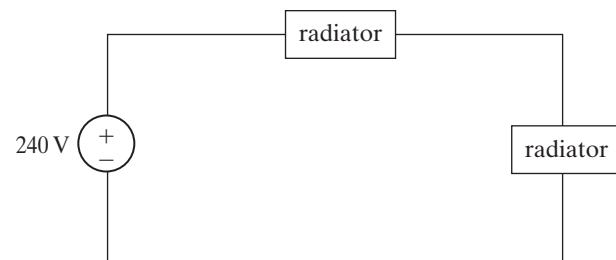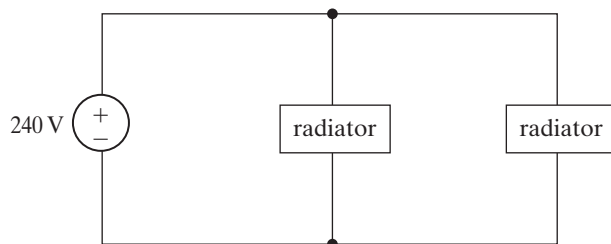

## 2.1 Voltage and Current Sources

An **electrical source** is a device capable of converting nonelectric energy to electric energy and vice versa. For example, a discharging battery converts chemical energy to electric energy, whereas a charging battery converts electric energy to chemical energy. A *dynamo* is a machine that converts mechanical energy to electric energy and vice versa. For operations in the mechanical-to-electric mode, it is called a *generator*. For transformations from electric to mechanical energy, it is called a *motor*. Electric sources either deliver or absorb electric power while maintaining either voltage or current. This behavior led to the creation of the ideal voltage source and the ideal current source as basic circuit elements.

- An **ideal voltage source** is a circuit element that maintains a prescribed voltage across its terminals regardless of the current flowing in those terminals.
- An **ideal current source** is a circuit element that maintains a prescribed current through its terminals regardless of the voltage across those terminals.

These circuit elements do not exist as practical devices—they are idealized models of actual voltage and current sources.

Using an ideal model for current and voltage sources constrains the mathematical descriptions of these components. For example, because an ideal voltage source provides a steady voltage even if the current in the element changes, it is impossible to specify the current in an ideal voltage source as a function of its voltage. Likewise, if the only information you have about an ideal current source is the value of current supplied, it is impossible to determine the voltage across that current source. We have sacrificed our ability to relate voltage and current in a practical source for the simplicity of using ideal sources in circuit analysis.


Ideal voltage and current sources can be further described as either *independent sources* or *dependent sources*.

- An **independent source** establishes a voltage or current in a circuit without relying on voltages or currents elsewhere in the circuit. The value of the voltage or current supplied is specified by the value of the independent source alone.
- A **dependent source**, in contrast, establishes a voltage or current whose value depends on the value of a voltage or current elsewhere in the circuit. You cannot specify the value of a dependent source unless you know the value of the voltage or current on which it depends.

The circuit symbols for the ideal independent sources are shown in Fig. 2.1. Note that a circle is used to represent an independent source. To completely specify an ideal independent voltage source in a circuit, you must include the value of the supplied voltage and the reference polarity, as shown in Fig. 2.1(a). Similarly, to completely specify an ideal independent current source, you must include the value of the supplied current and its reference direction, as shown in Fig. 2.1(b).


The circuit symbol for an ideal dependent source is a diamond, as shown in Fig. 2.2. There are four possible variations because both dependent current sources and dependent voltage sources can be controlled by either a voltage or a current elsewhere in the circuit. Dependent sources are sometimes called controlled sources.

To completely specify an ideal dependent voltage-controlled voltage source, you must identify the controlling voltage, the equation that

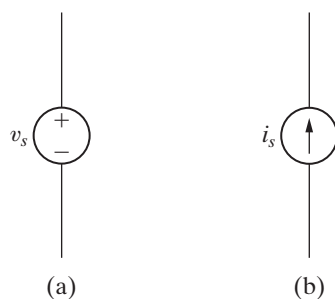

**Figure 2.1** ▲ The circuit symbols for (a) an ideal independent voltage source and (b) an ideal independent current source.



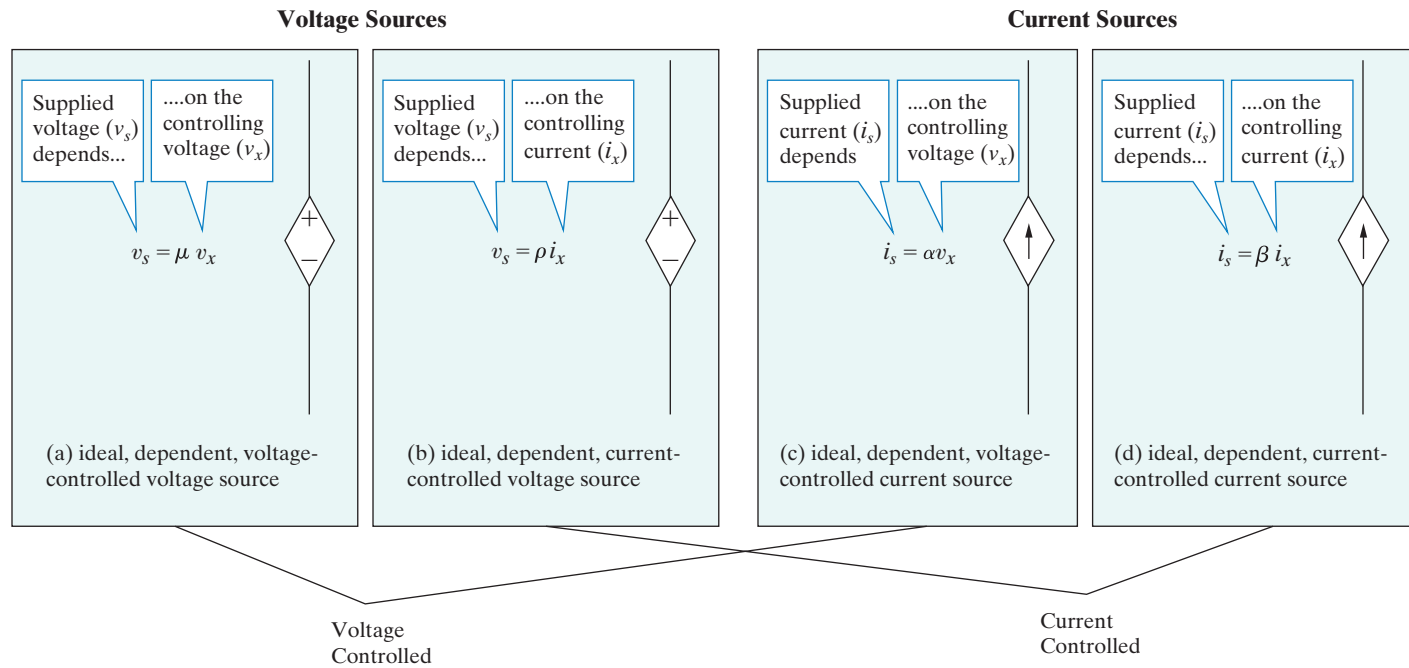

**Figure 2.2** ▲ (a) (b) Circuit symbols for ideal dependent voltage sources and (c) (d) ideal dependent current sources.

permits you to compute the supplied voltage from the controlling voltage, and the reference polarity for the supplied voltage. For example, in Fig. 2.2(a), the controlling voltage is  $v_x$ , the equation that determines the supplied voltage  $v_s$  is

$$v_s = \mu v_x,$$

and the reference polarity for  $v_s$  is as indicated. Note that  $\mu$  is a multiplying constant that is dimensionless.

Similar requirements exist for completely specifying the other ideal dependent sources. In Fig. 2.2(b), the controlling current is  $i_x$ , the equation for the supplied voltage  $v_s$  is

$$v_s = \rho i_x,$$

the reference polarity is as shown, and the multiplying constant  $\rho$  has the dimension volts per ampere. In Fig. 2.2(c), the controlling voltage is  $v_x$ , the equation for the supplied current  $i_s$  is

$$i_s = \alpha v_x,$$

the reference direction is as shown, and the multiplying constant  $\alpha$  has the dimension amperes per volt. In Fig. 2.2(d), the controlling current is  $i_x$ , the equation for the supplied current  $i_s$  is

$$i_s = \beta i_x,$$

the reference direction is as shown, and the multiplying constant  $\beta$  is dimensionless.

Note that the ideal independent and dependent voltage and current sources generate either constant voltages or currents, that is, voltages and